

Experiment no: 04

Name of the experiment: Designing Multiplexer  
(Mux) Demultiplexer (DEMux), Encoder,  
Decoder circuit

Group no: 03

Student Name: Sheikh Muhtasim Nasir

Student ID: 20-42119-1

Course Title: Digital Logic and Circuit Lab

Section: M

Date of experiment: 16.06.2022

Date of Submission: 21.06.2022


### Objective:

- (i) Design 4 to 1 multiplexer and verify the truth table
- (ii) Design 8 to 4 ~~multiplexer~~ demultiplexer and verify the truth table
- (iii) Design Decimal to BCD encoder and verify the truth table
- (iv) Design 2 to 4 line decoder and verify the truth table.

### List of components:


NOT gate: IC 7404  
AND gate: IC 7408  
OR gate: ~~IC 7401~~  
(i) 3 input OR

Symbols, Block diagram and Figures:

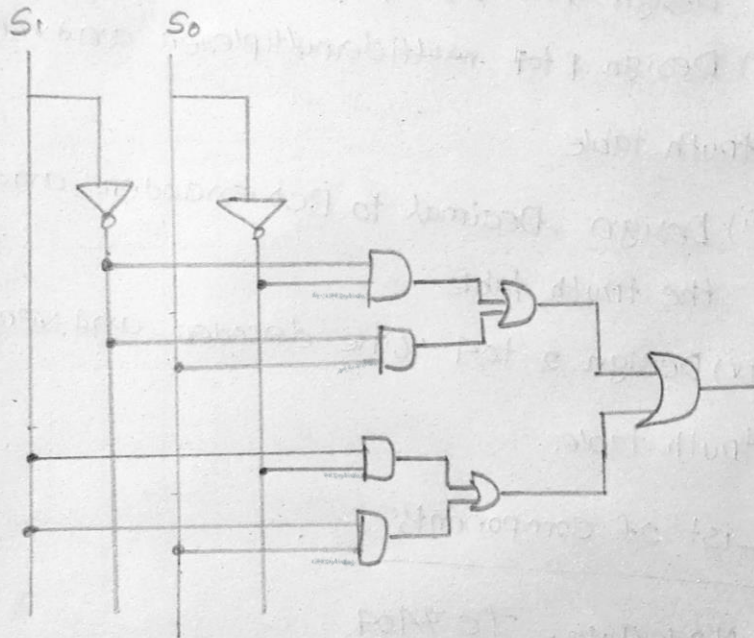


4-to-1 Multiplexer




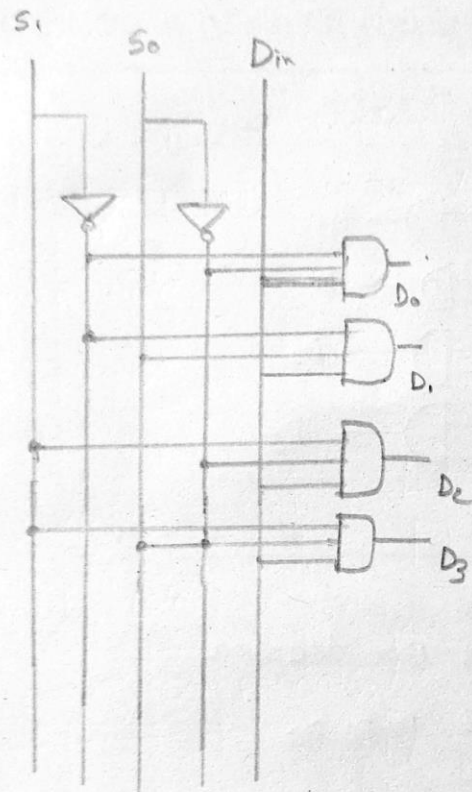

1 to 4 Demultiplexer

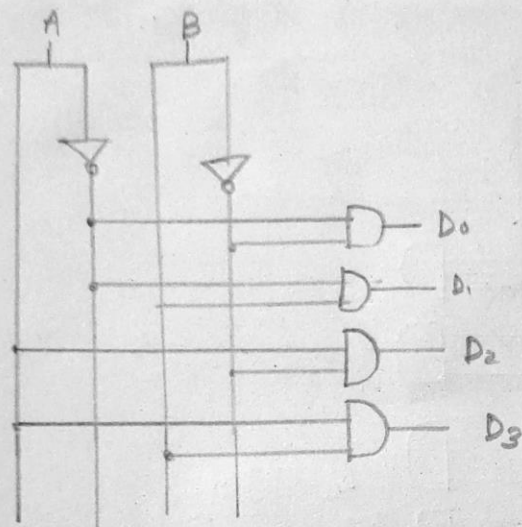

2 to 4 line decoder

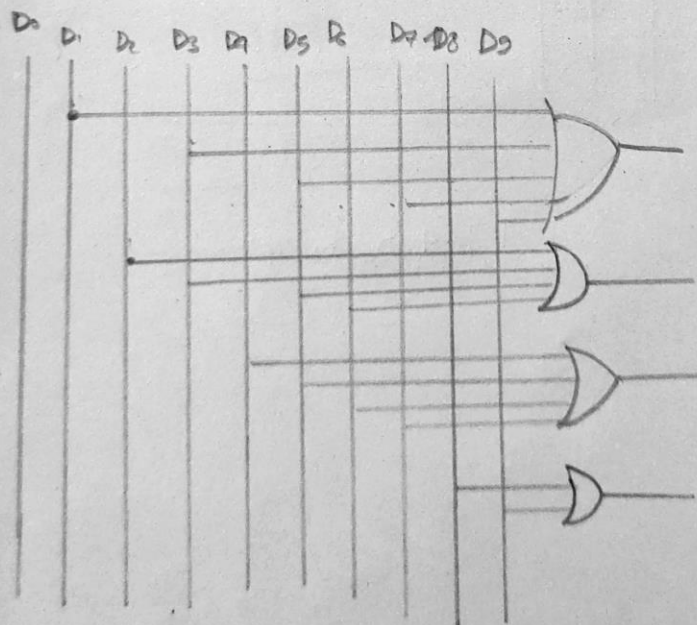

Decimal to BCD encoder

Data table and Calculation:

4 to 1 Mux

$S_1$	$S_0$	$f$
0	0	$D_0$
0	1	$D_1$
1	0	$D_2$
1	1	$D_3$

~~$$f = \bar{S}_1 \bar{S}_0 D_0 + \bar{S}_1 S_0 D_1 + S_1 \bar{S}_0 D_2 + S_1 S_0 D_3$$~~

$$f = \bar{S}_1 \bar{S}_0 D_0 + \bar{S}_1 S_0 D_1 + S_1 \bar{S}_0 D_2 + S_1 S_0 D_3$$

1 to 4 Demux

$S_1$	$S_0$	$D_0$	$D_1$	$D_2$	$D_3$
0	0	$D_{in}$	0	0	0
0	1	0	$D_{in}$	0	0
1	0	0	0	$D_{in}$	0
1	1	0	0	0	$D_{in}$

$$D_0 = \bar{S}_1 \bar{S}_0 D_{in}$$

$$D_1 = \bar{S}_1 S_0 D_{in}$$

$$D_2 = S_1 \bar{S}_0 D_{in}$$

$$D_3 = S_1 S_0 D_{in}$$



### Decimal to BCD Encoder

Dec	$Y_3$	$Y_2$	$Y_1$	$Y_0$
$D_0$	0	0	0	0
$D_1$	0	0	0	1
$D_2$	0	0	1	0
$D_3$	0	0	1	0
$D_4$	0	1	0	0
$D_5$	0	1	0	1
$D_6$	0	1	1	0
$D_7$	0	1	1	1
$D_8$	1	0	0	0
$D_9$	1	0	0	1

$$Y_0 = D_1 + D_3 + D_5 + D_7 + D_9$$

$$Y_1 = D_2 + D_3 + D_6 + D_7$$

$$Y_2 = D_4 + D_5 + D_6 + D_7$$

$$Y_3 = D_8 + D_9$$

### 2 to 4 line decoder

A	B	D <sub>0</sub>	D <sub>1</sub>	D <sub>2</sub>	D <sub>3</sub>
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

$$D_0 = \bar{A}\bar{B}$$

$$D_1 = \bar{A}B$$



$$D_2 = A\bar{B}$$



$$D_3 = AB$$






# Simulation

## 4 to 1 MUX

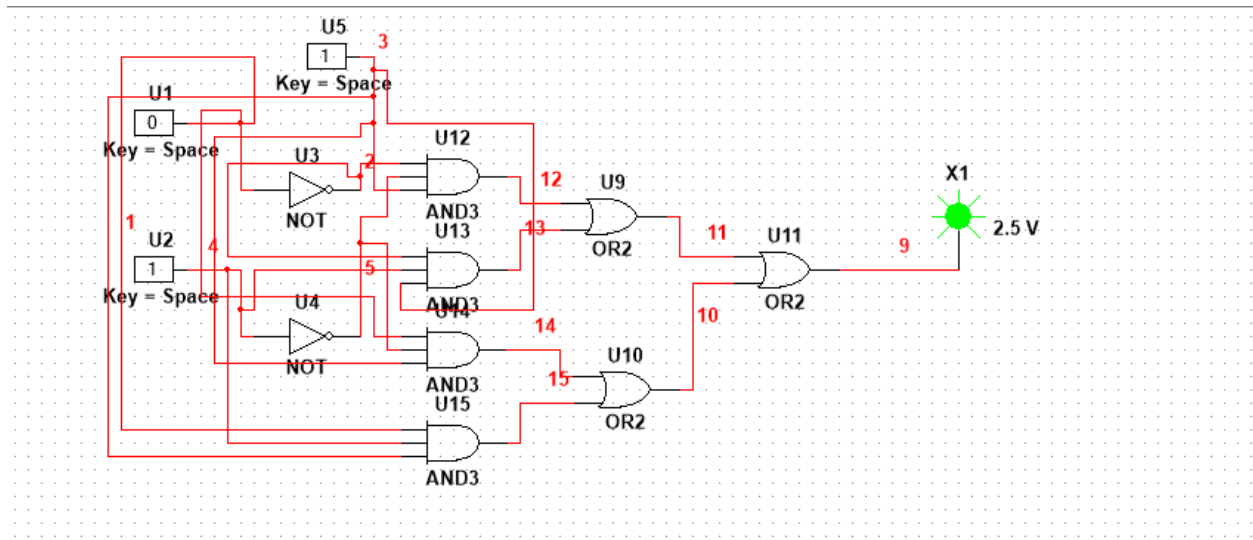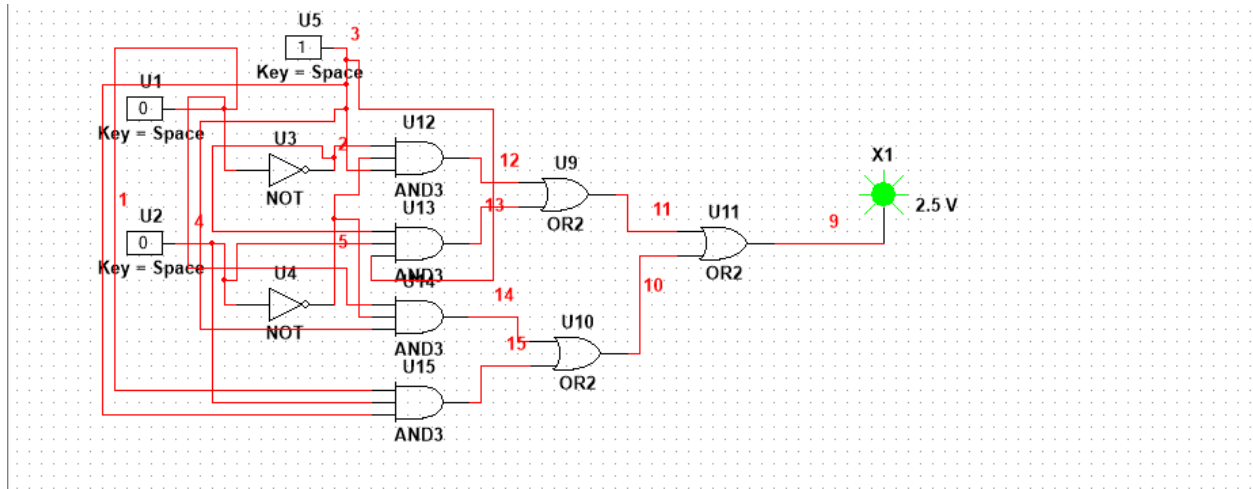


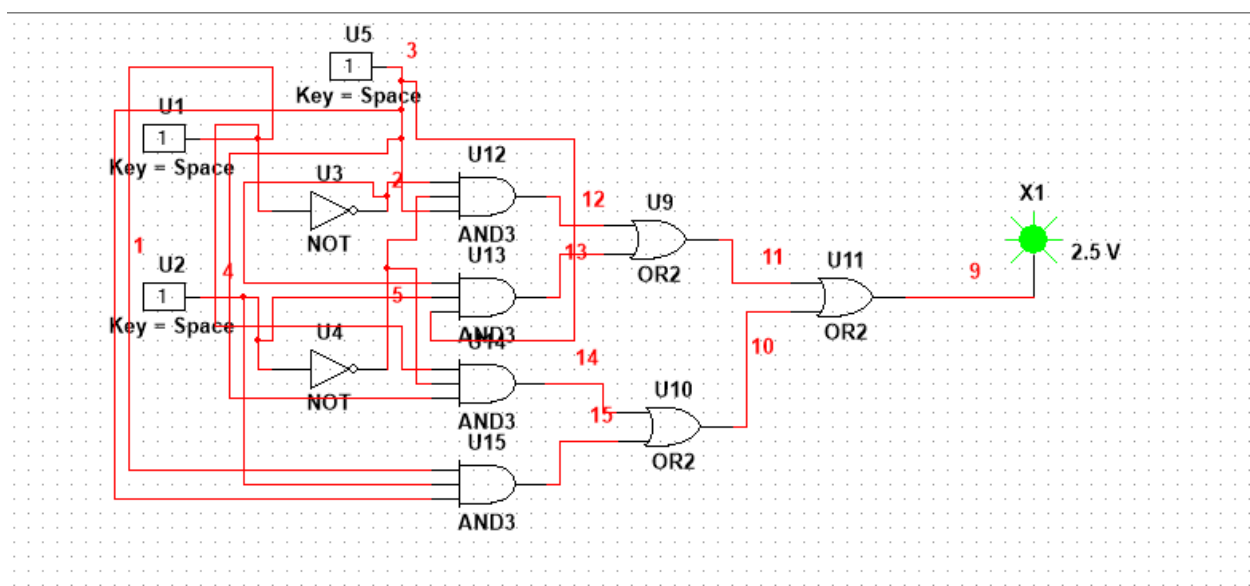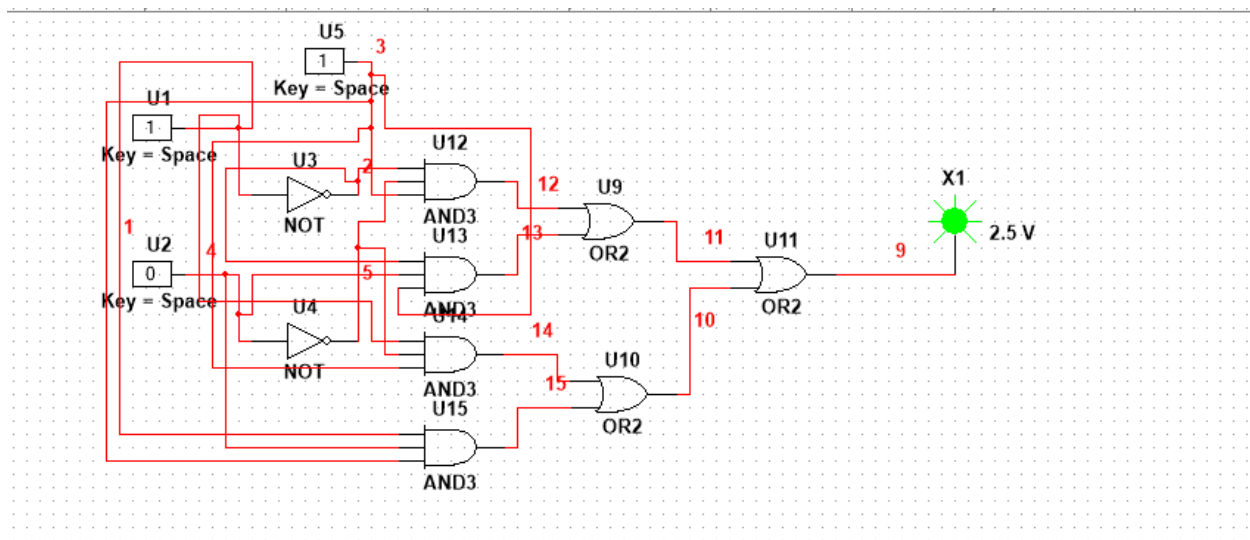


1 to 4 DEMUX

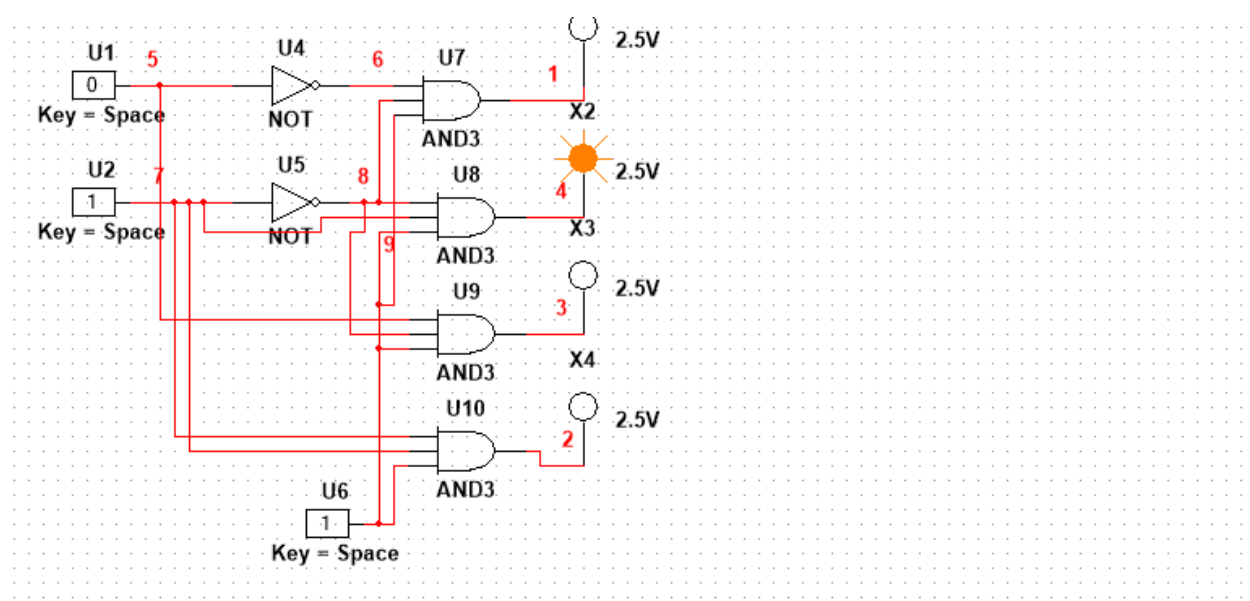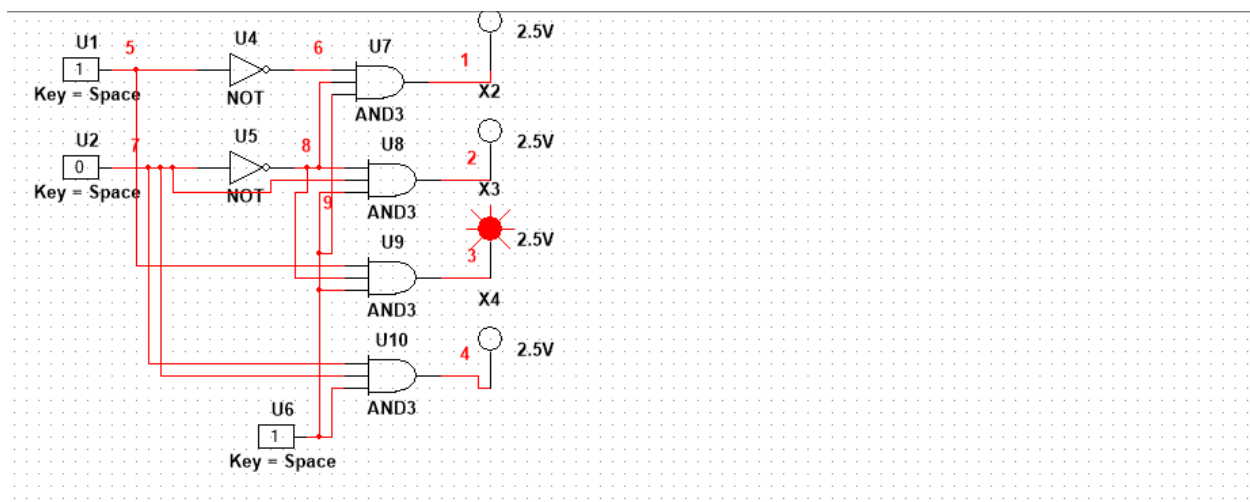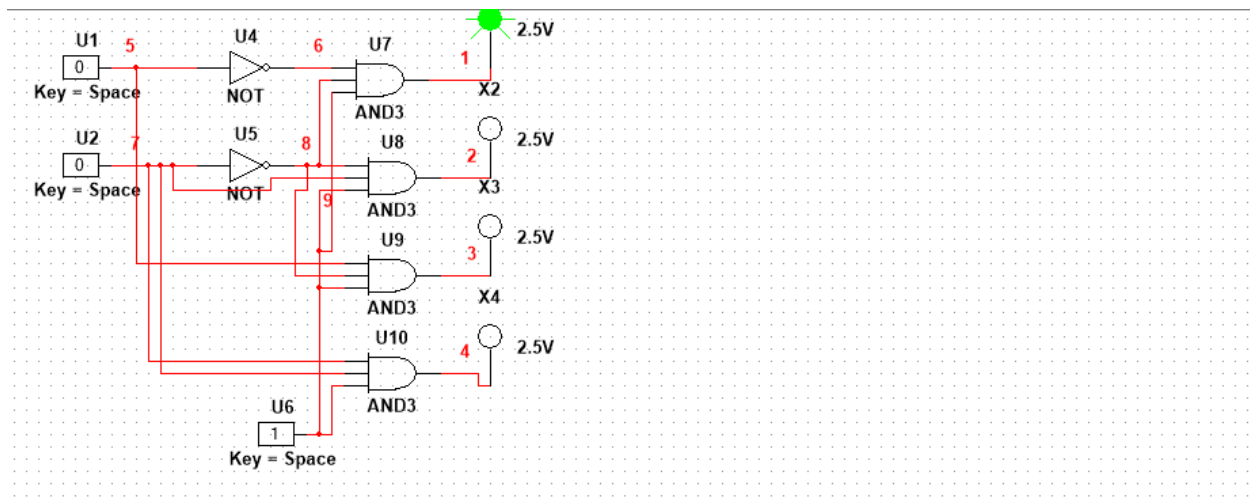





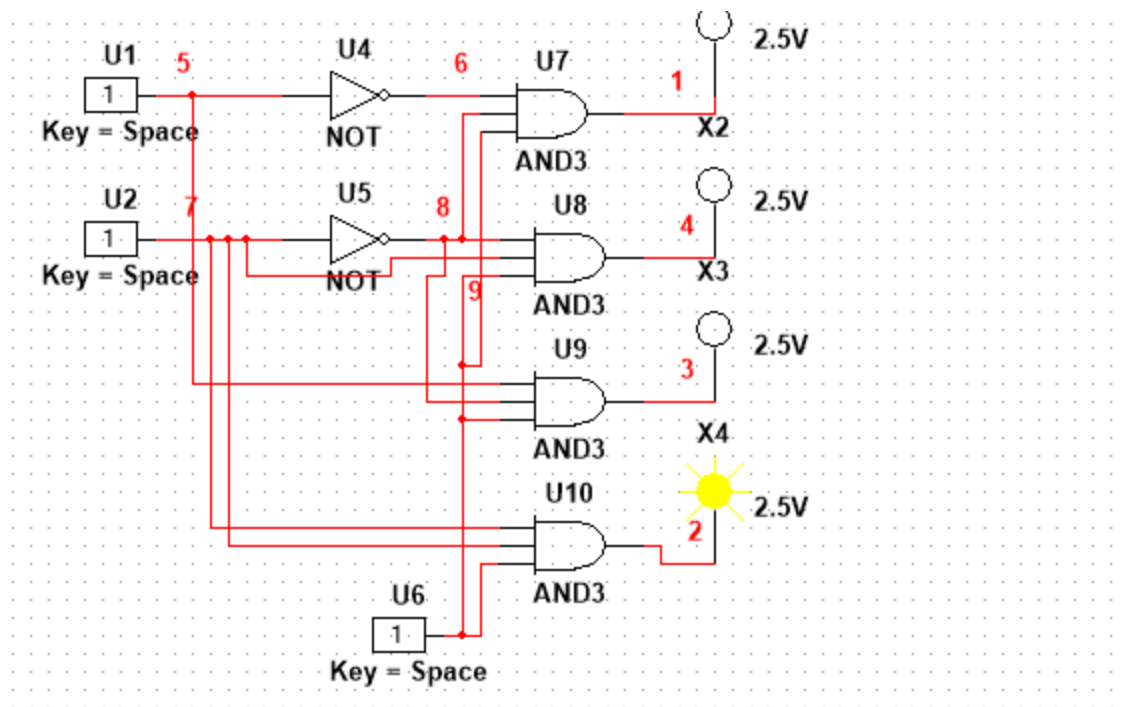

2 to 4 line decoder



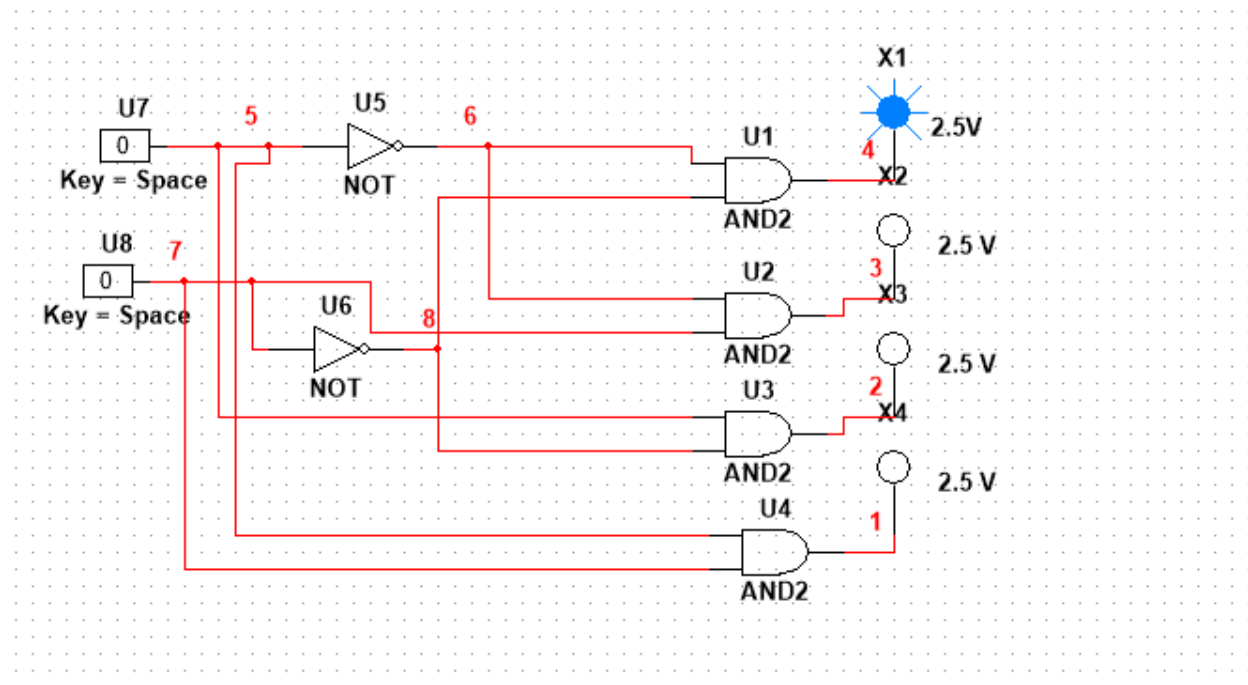


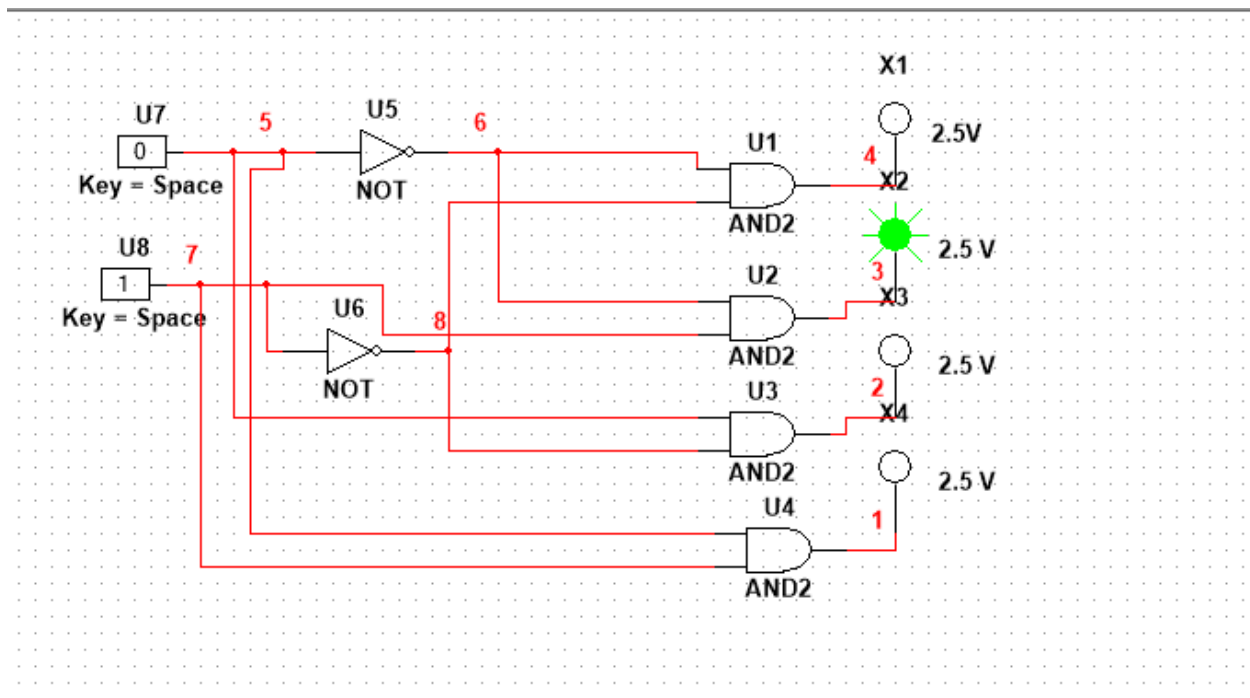


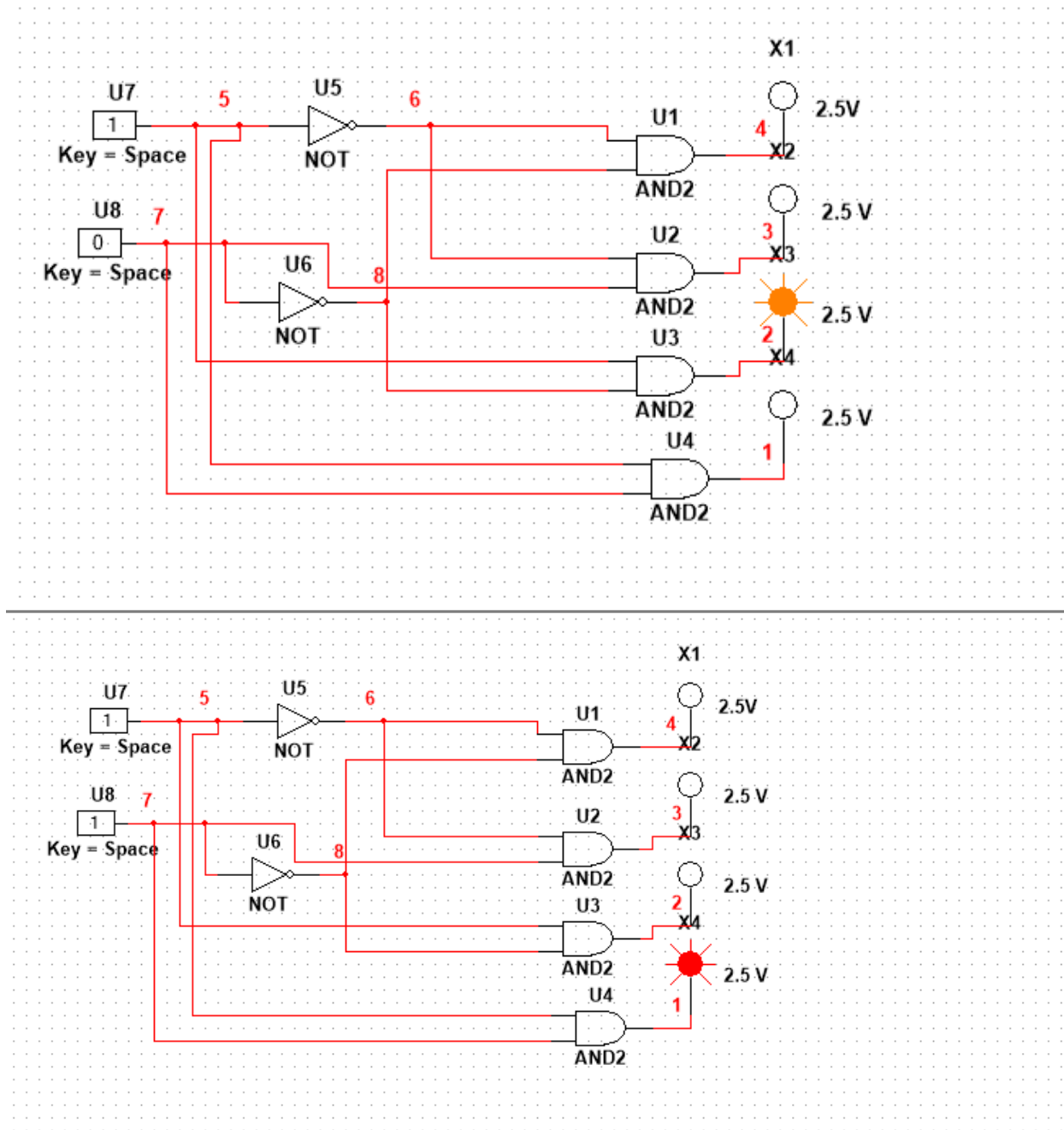

Decimal to BCD encoder



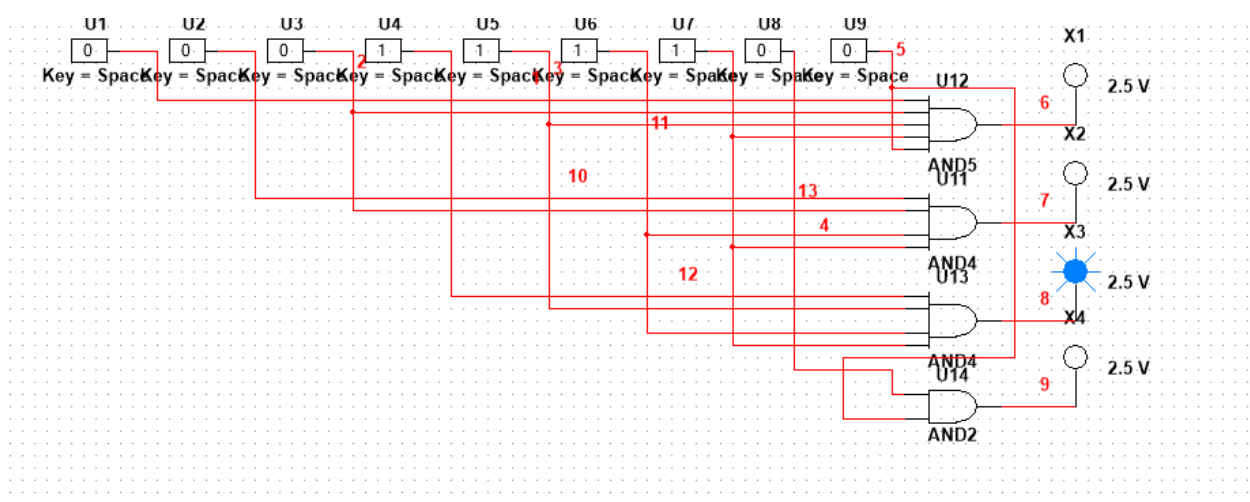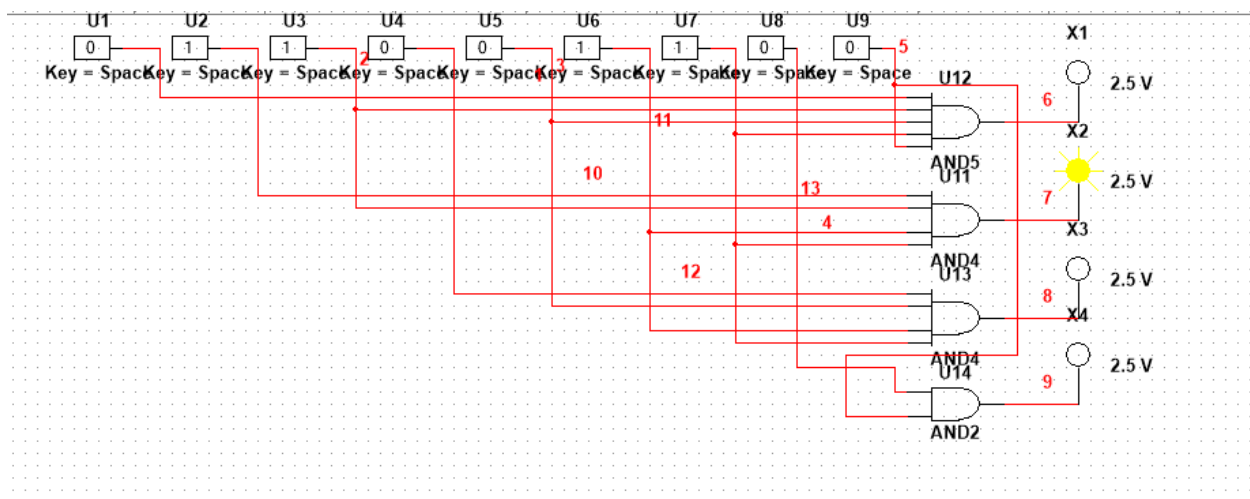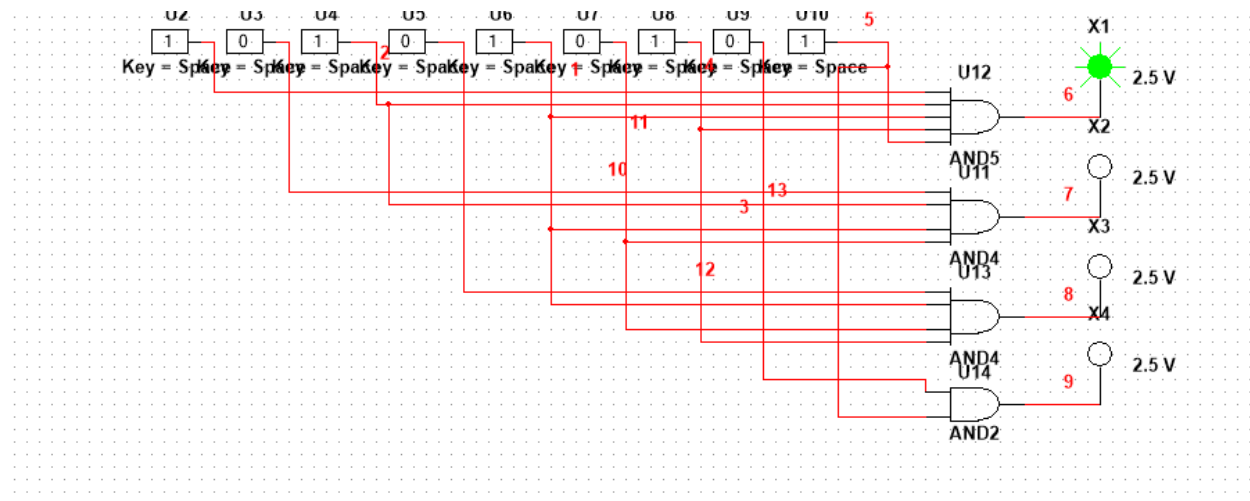

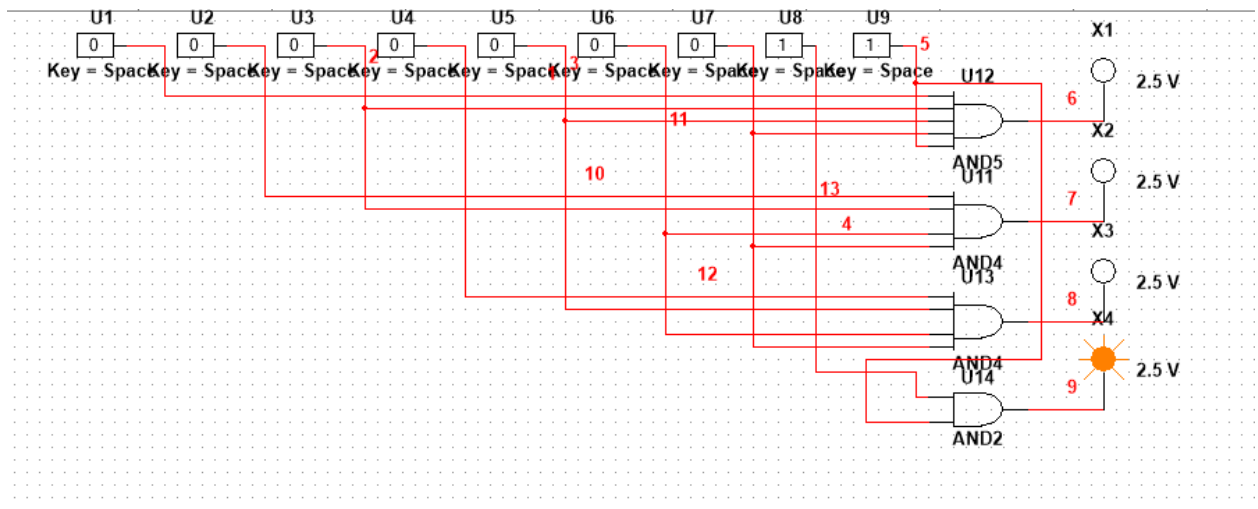

### Discussion:

A mux is a device which selects one of several inputs and forwards the selected input into a single line. A demux is single input taking and provide many output line. Encoder and decoders are mainly used for encode and decode a digital signal.

In the experiments we mainly verify the truth tables using some IC's. There some inputs where for 3 bit, some were for 2 bits. 3 bits input has various pin configuration. By applying the circuit, we have find out the output.

During experiment, there were some errors in IC pins. Due to excessive use, some pins were not working properly. Despite all of this, the experiment were success as we have matched the output and that's why the experiment success is achieved.



### Conclusion:

To verify mux, demux, decoder, encoder, we mainly used OR gate, AND gate and NOT gate i.e. we solved a boolean function for the truth table. The output was verified.

### Remarks:

- (i) Mux are mainly used for computer memory, telephone networks, etc
- (ii) Demux are used for mainly carrying multiple data signal
- (iii) Encoder and decoder are used for data encryption, decryption

### Reference:

- [1] Thomas L. Floyd "Digital Fundamentals" 11th edition