

Experiment: 03:

Name of the experiment: Design of Adder,  
subtractor and comparator circuit.

Group no: 03

Student name: Sheikh Muhtasim Nasir

Student id: 20 - 42119 - 1

Course title: Digital Logic and Circuit Lab

Section: M

Date of experiment: 09/06/2022

Date of Submission: 15/06/2022

### Objective of the experiment:

- (i) To see how adder, subtractor and comparator works and verify the truth table
- (ii) Observing the application of integral circuit
- (iii) To make complex circuit from boolean expression


### List of components:

- (i) Trainer board
- (ii) IC
- (iii) Wires

#### IC:

IC 7408  
IC 7432  
IC 7404  
IC 7486  
IC 74

Symbol, block diagram and figures:

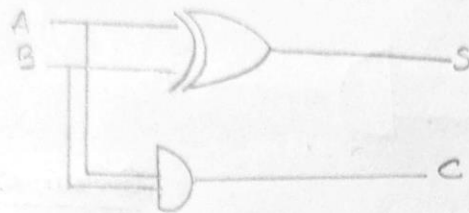


Half adder

Boolean expression

$$S = A \oplus B$$

$$C = AB$$

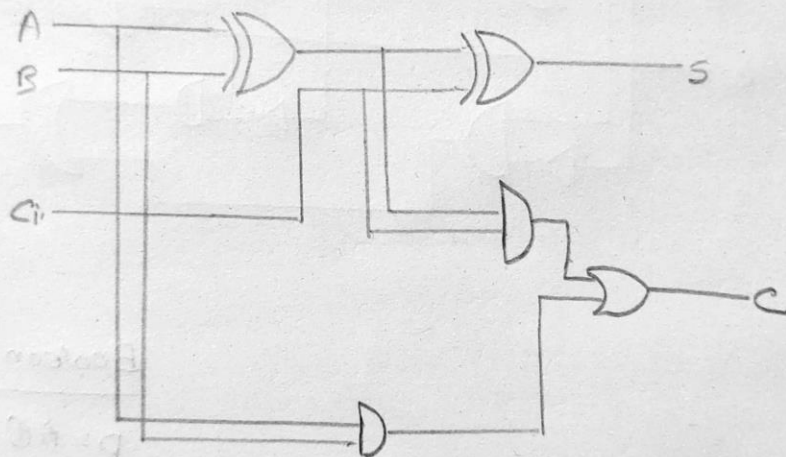


Boolean -

$$S = A \oplus B \oplus C_{in}$$

$$C = C_{in}(A \oplus B) + AB$$

Full adder



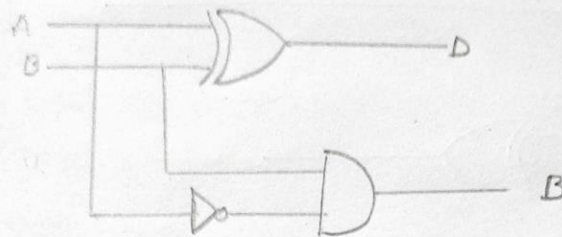


Half Subtractor

Boolean expression

$$D = A \oplus B$$

$$B = AB$$

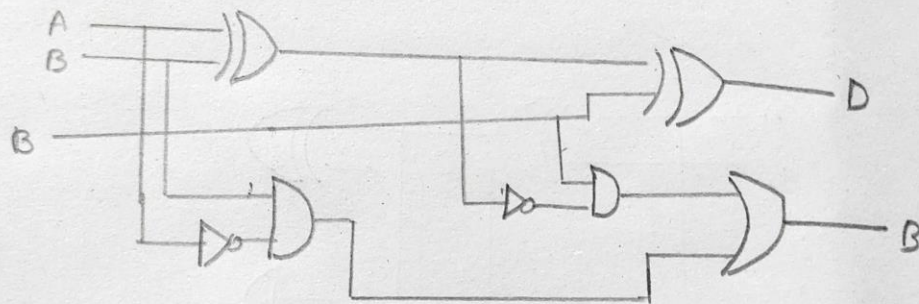


Full Subtractor.


Boolean Expression

$$D = A \oplus B \oplus C$$

$$Bout = AB + \bar{A}B + B\bar{C}$$

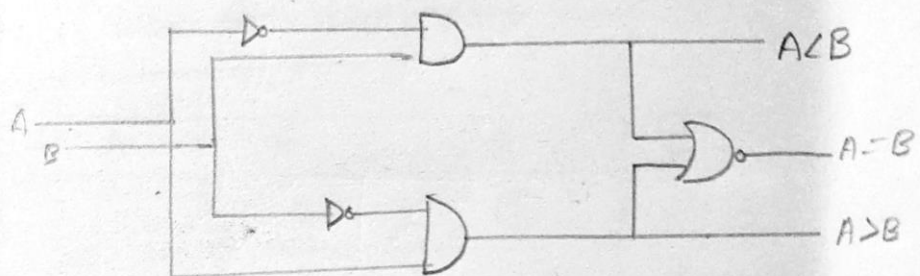

1 Bit comparator.

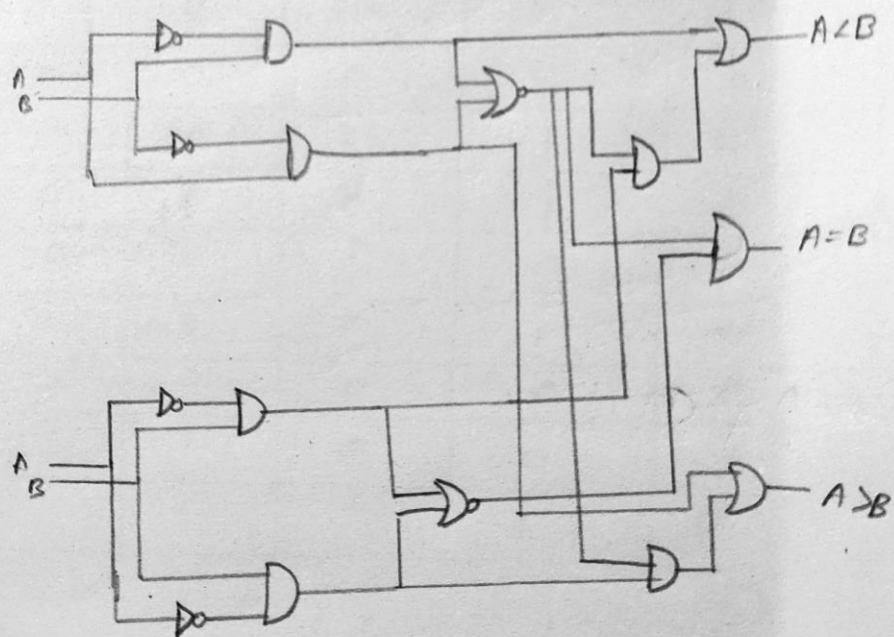

2 bit comparator

Data table:

Truth table for Half adder:

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Truth table for Full adder:

A	B	Cin	S	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	0
1	0	0	1	0
1	0	1	0	0
1	1	0	0	1
1	1	1	1	0



Half subtraction:


A	B	D	B
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Full Subtraction:



A	B	Bin	D	Bout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	0

## Simulation




### Half Adder Simulation:


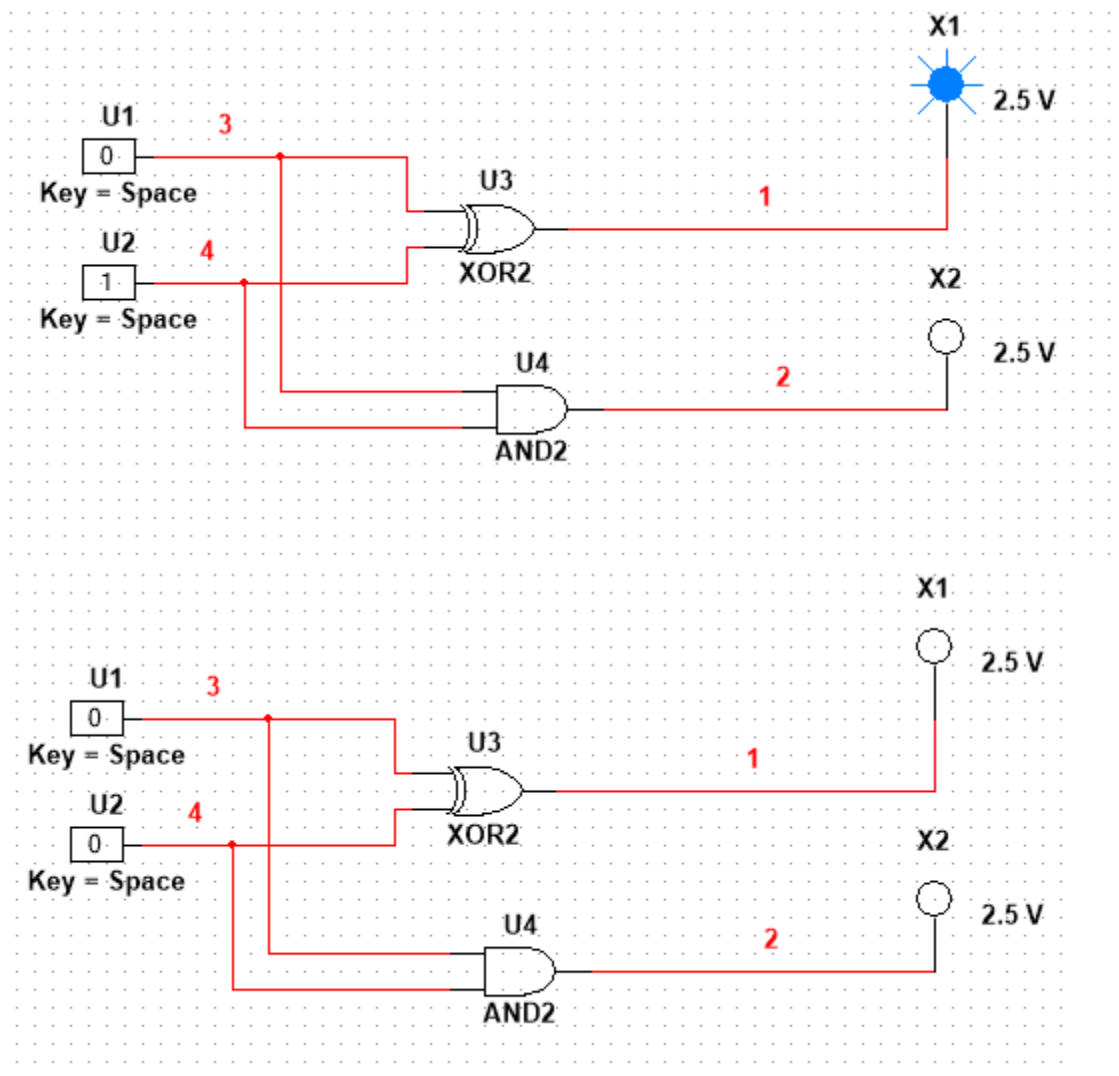





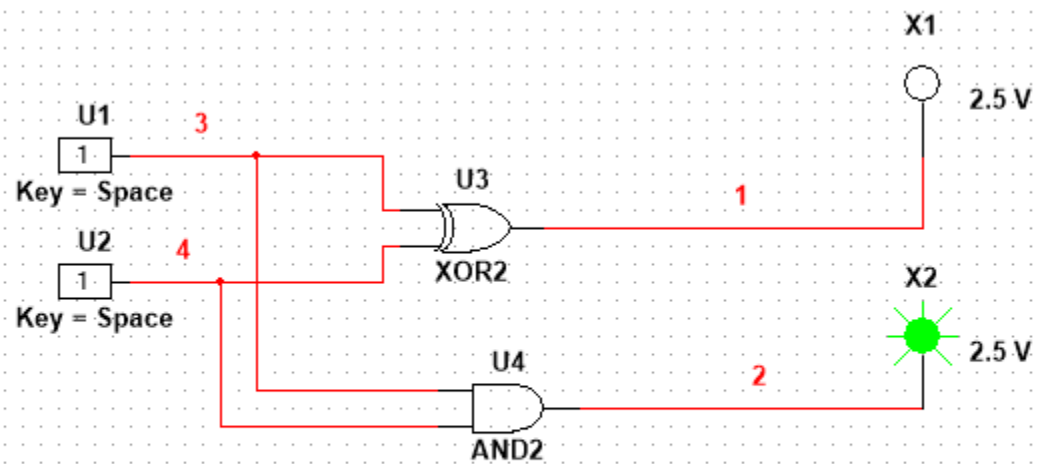
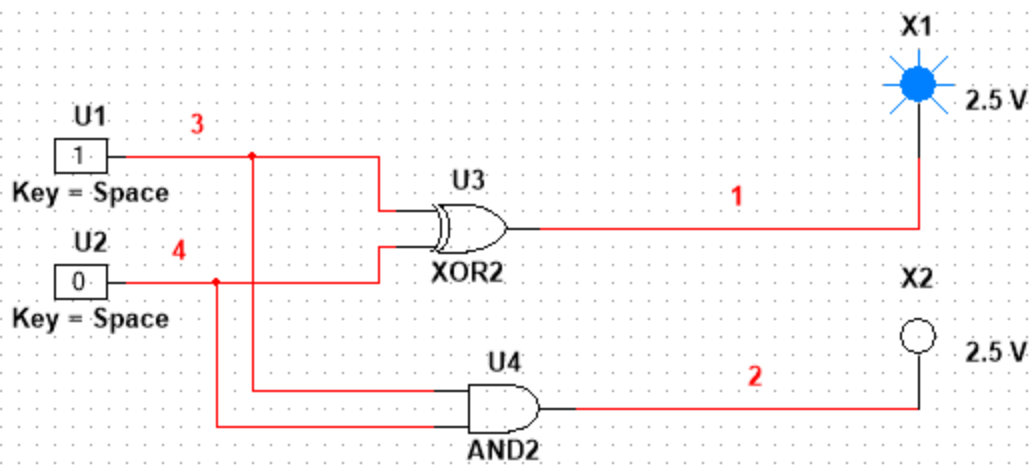


## Full Adder Simulation:

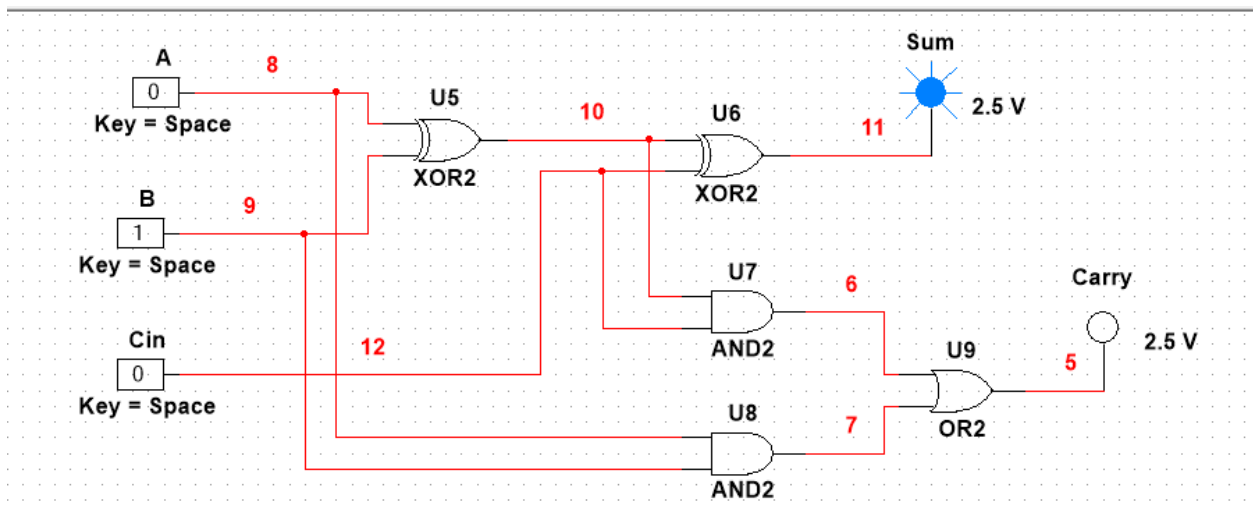
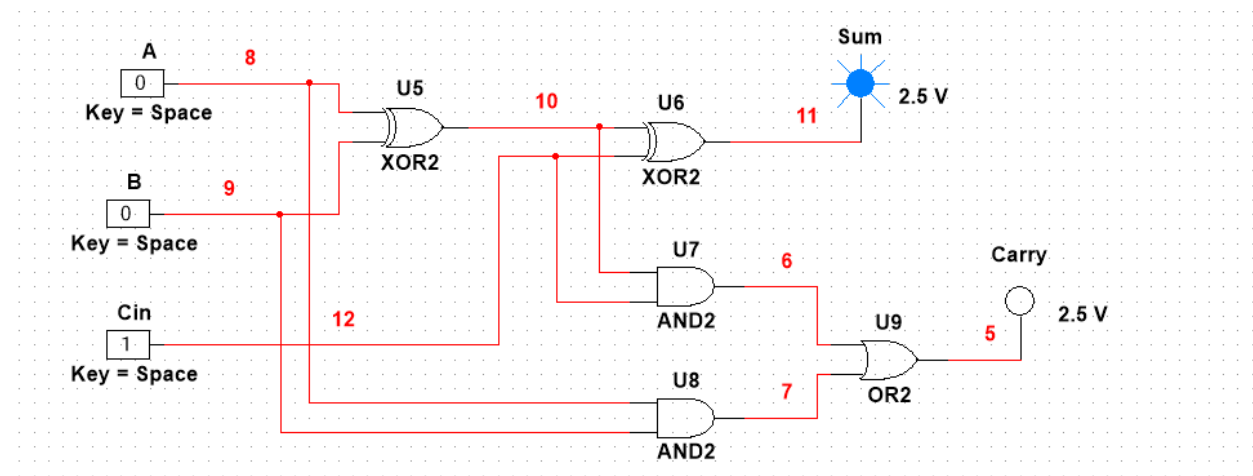
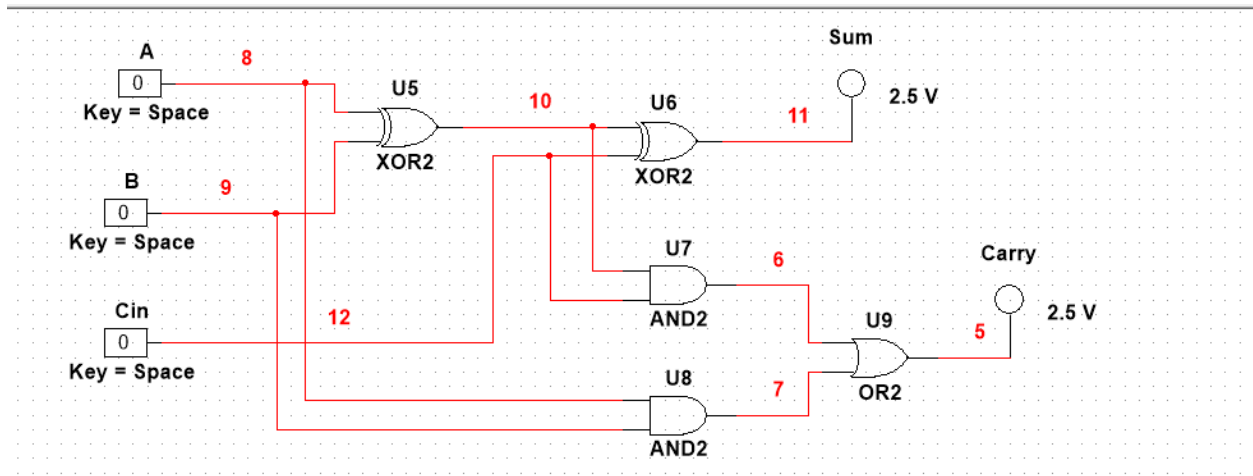


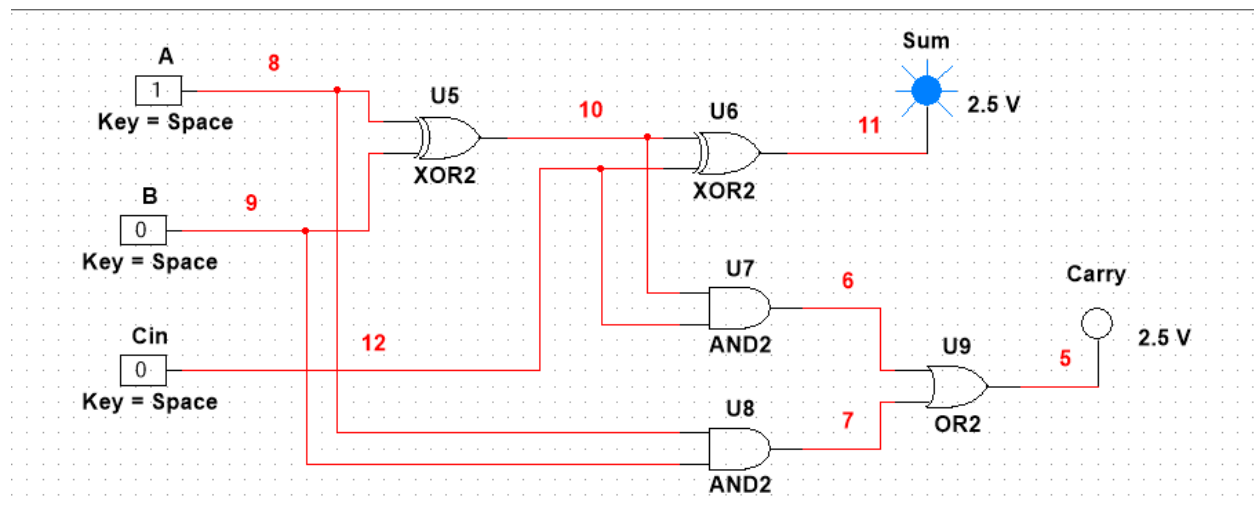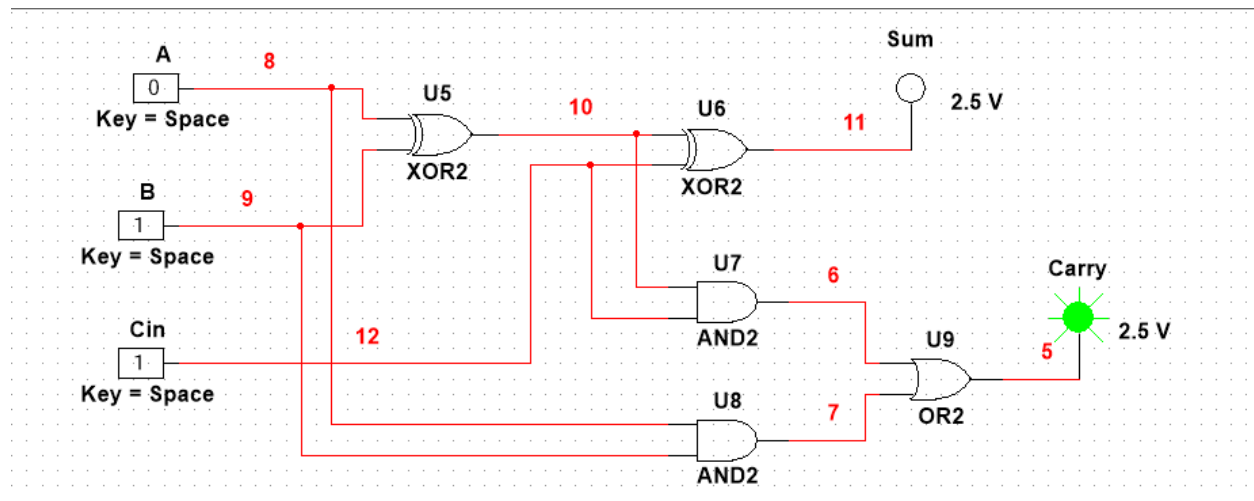




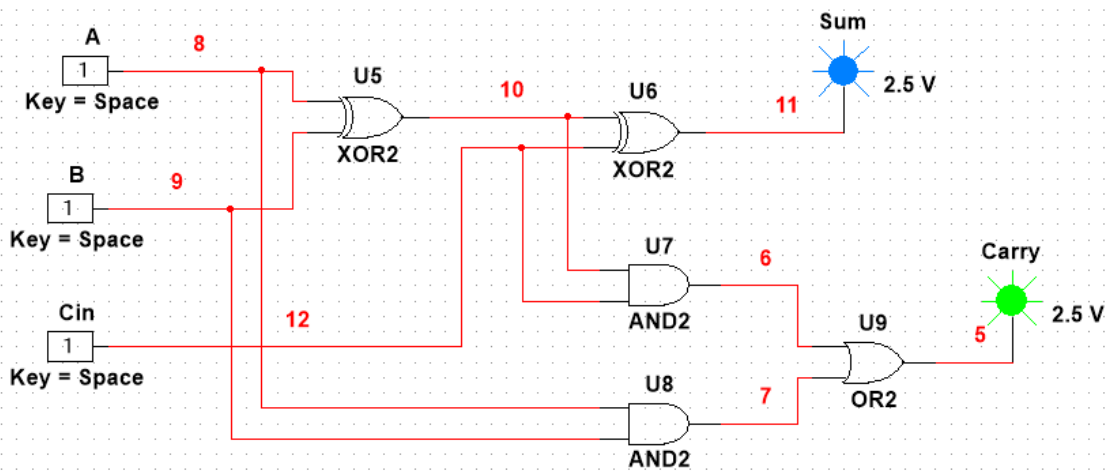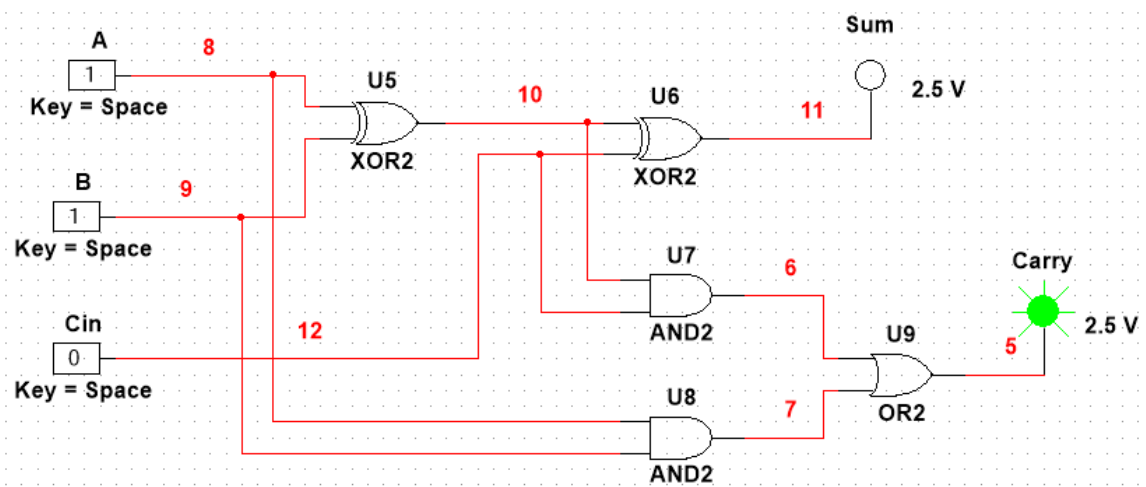
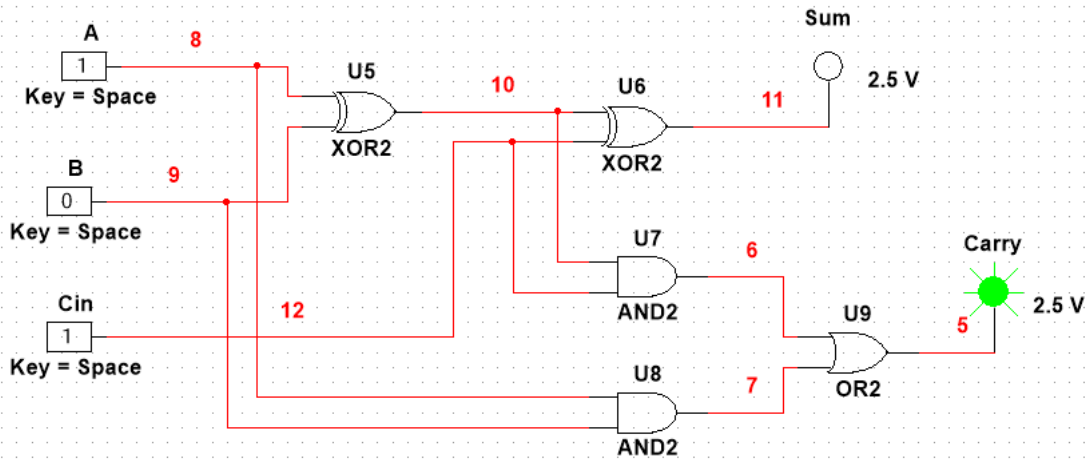


Half Subtractor:

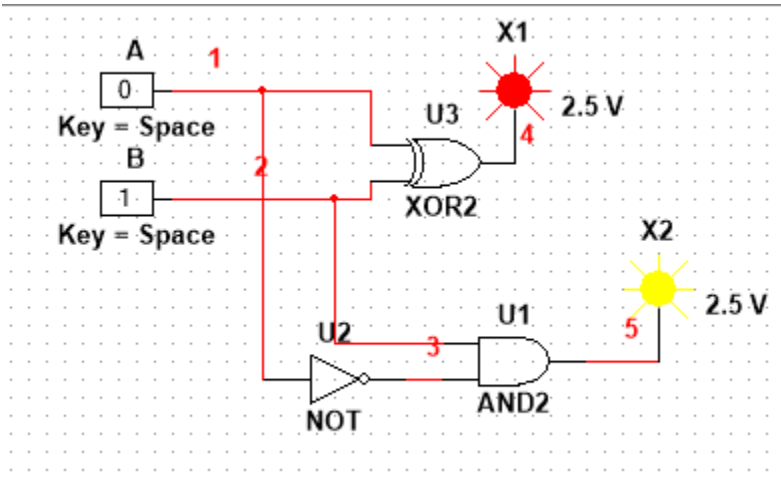
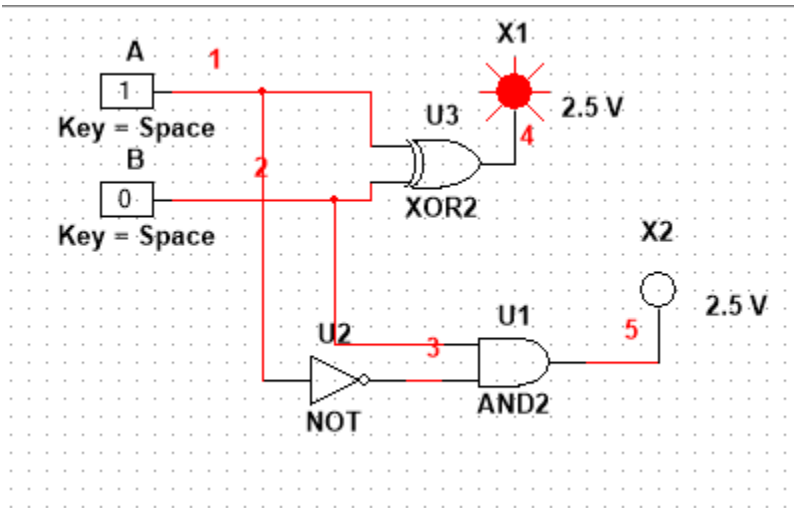
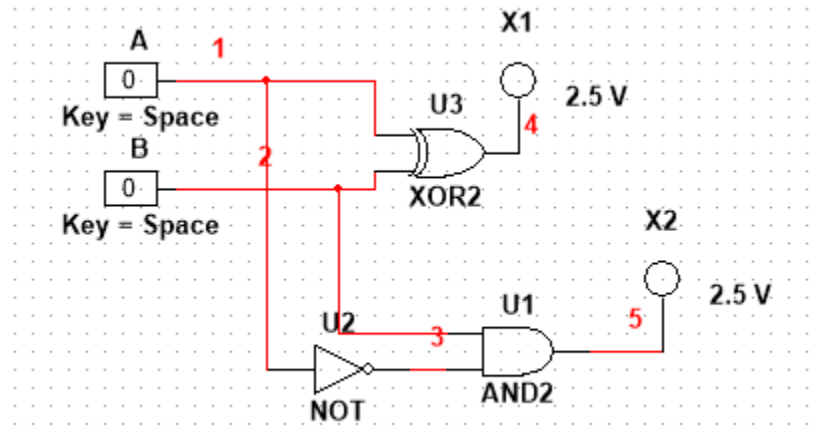




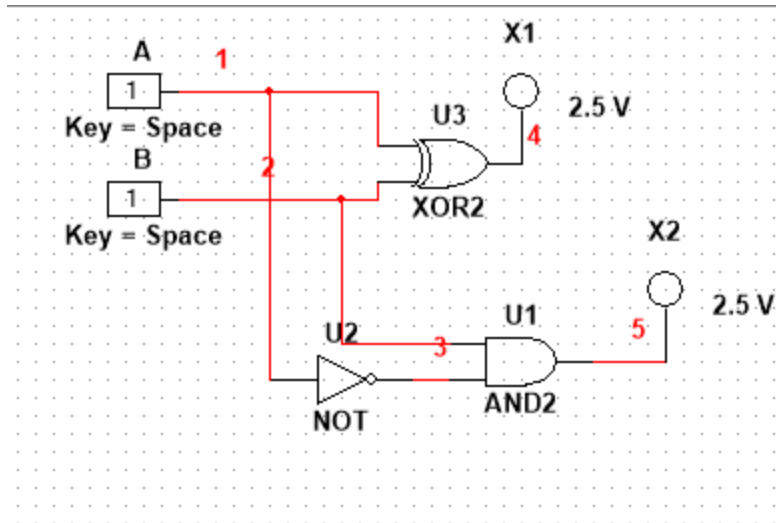


Full Subtractor:

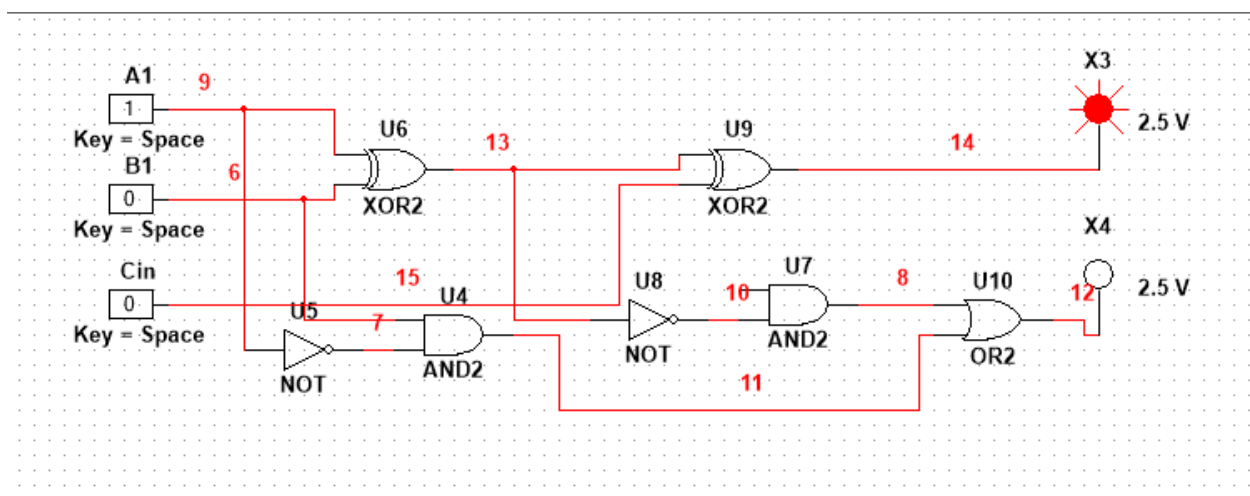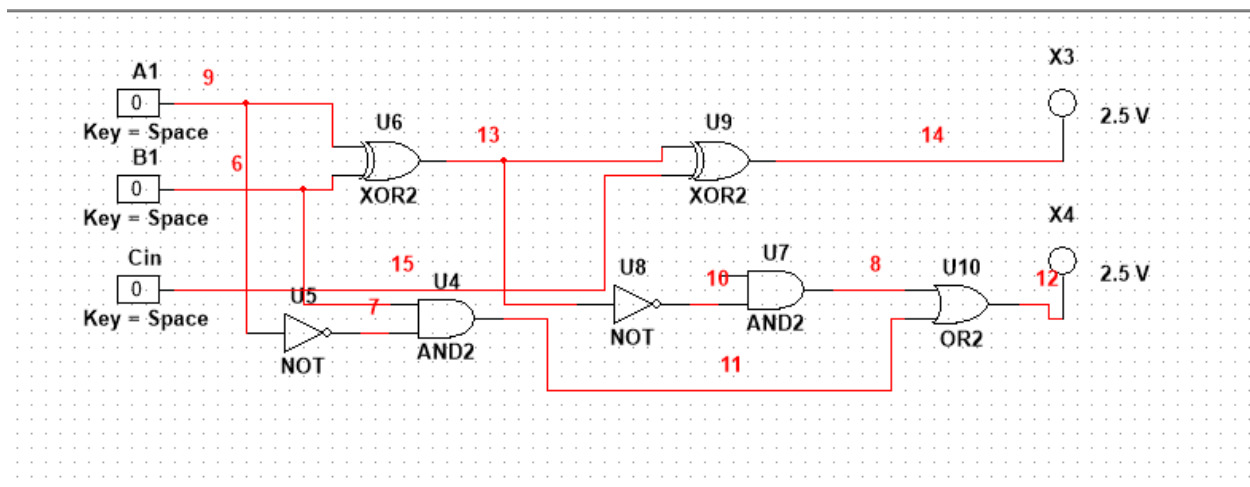




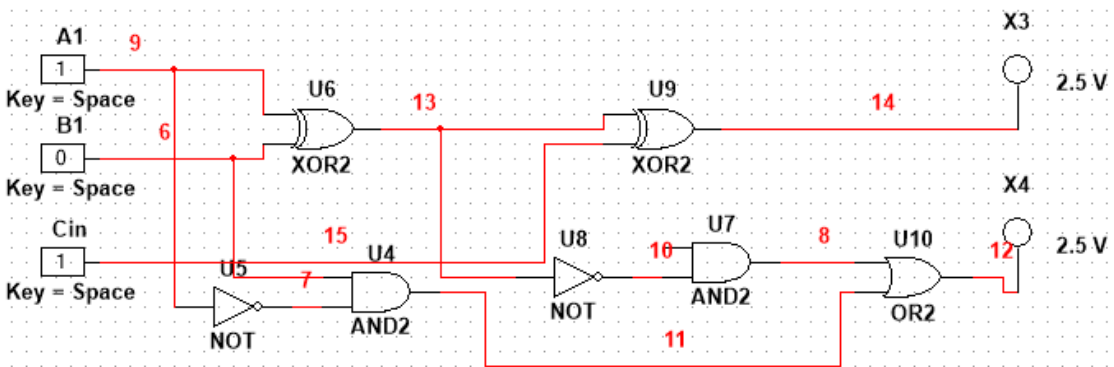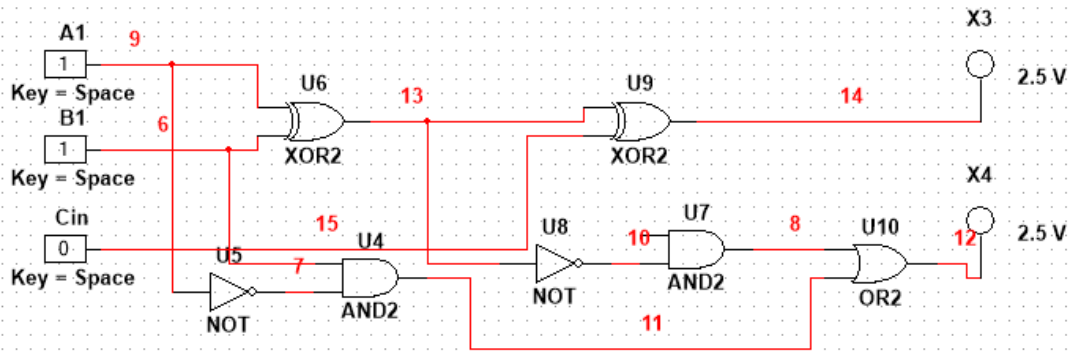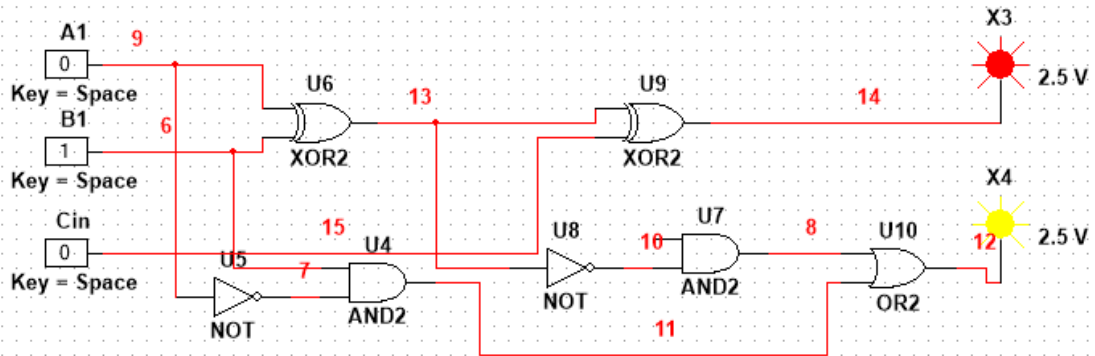


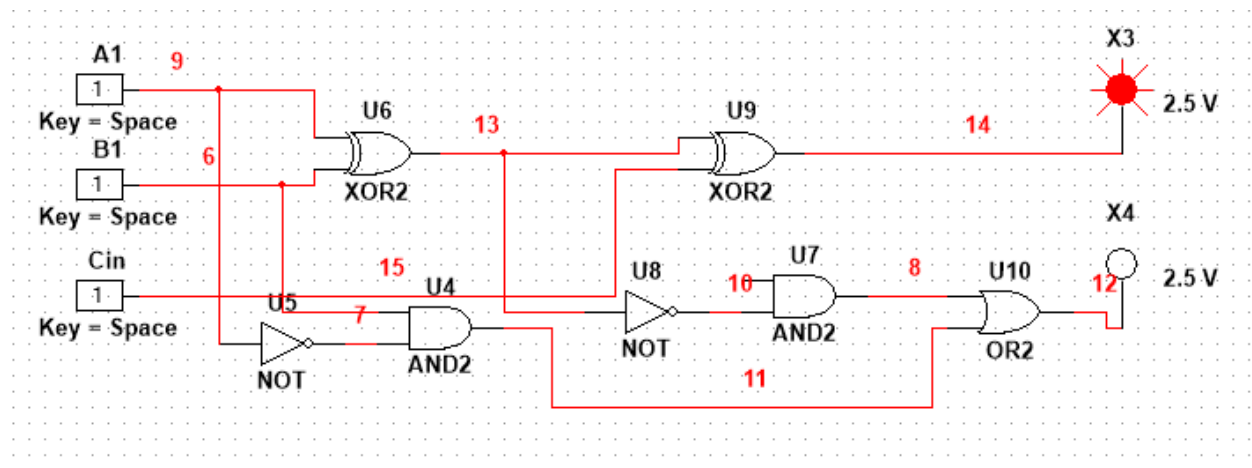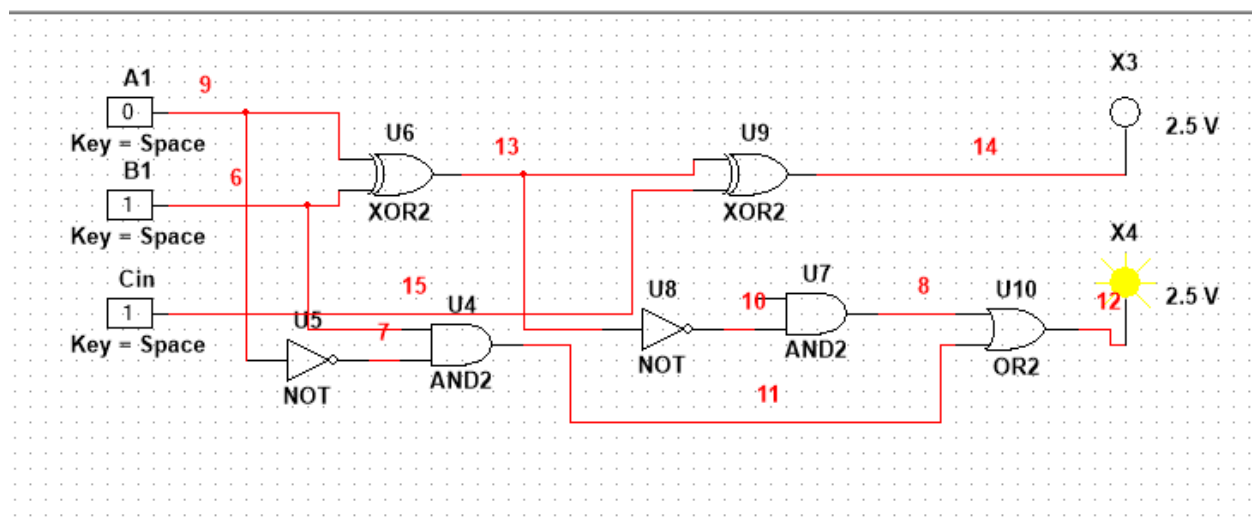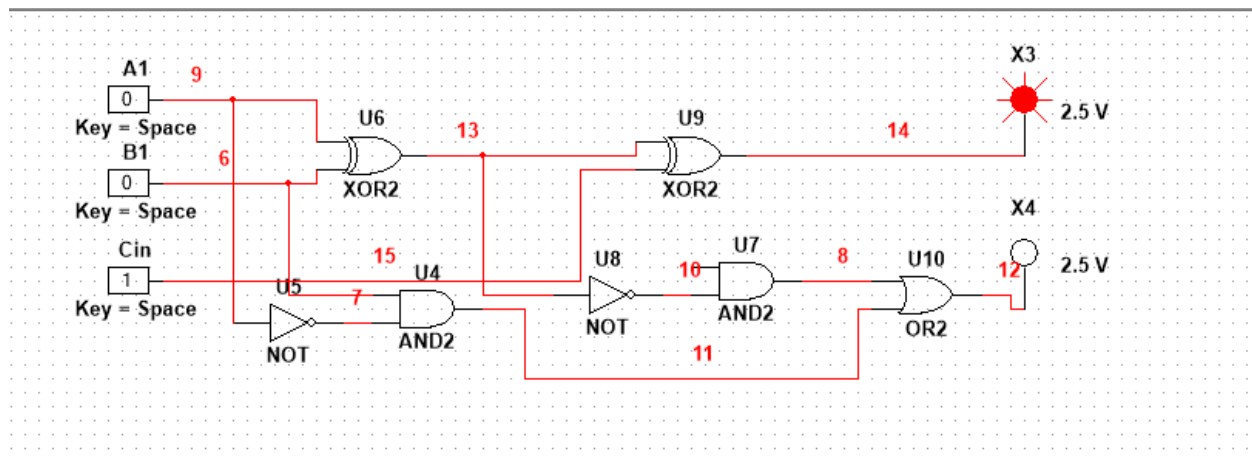


## 1 bit Comparator:



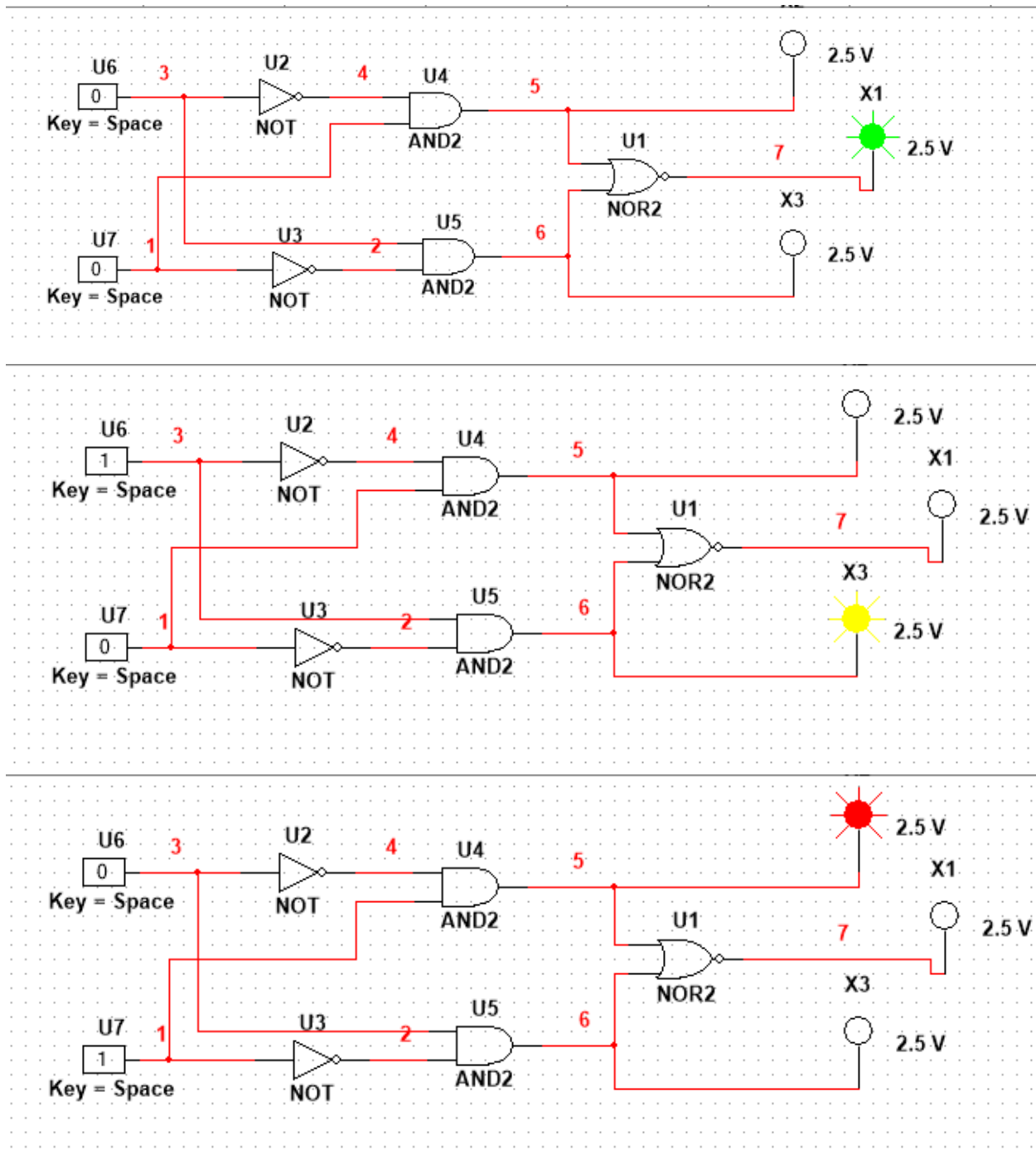







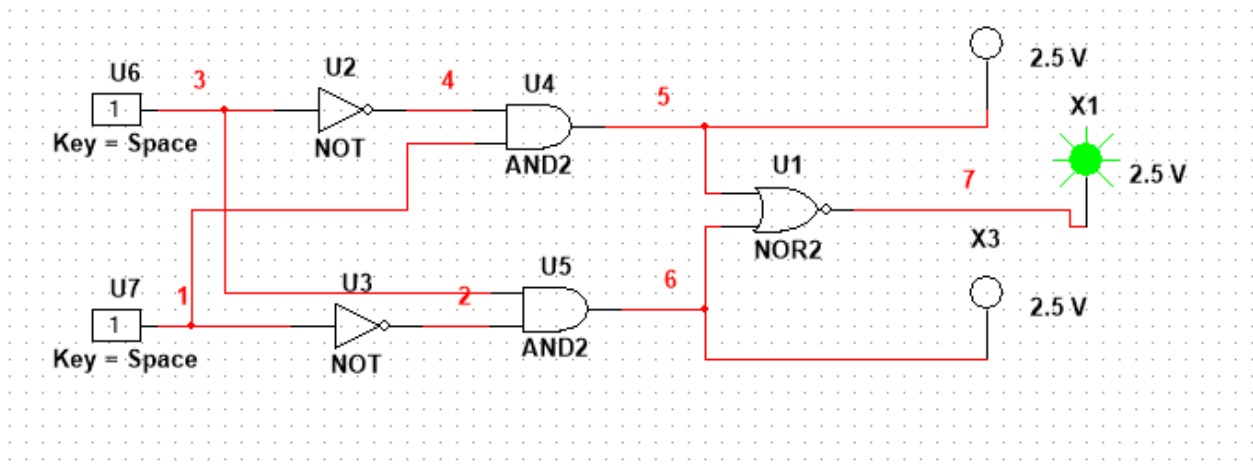




## 2-bit Comparator:



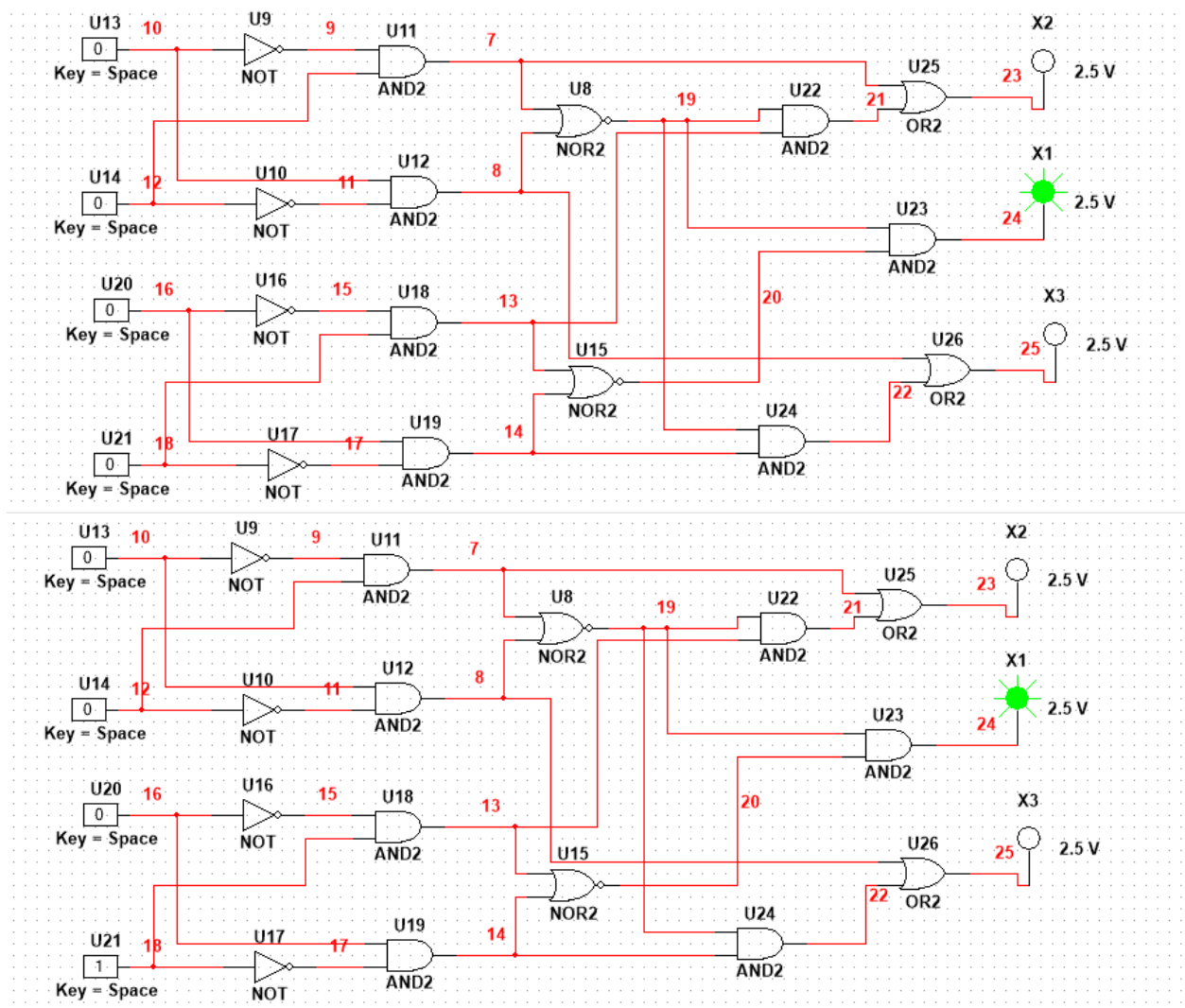


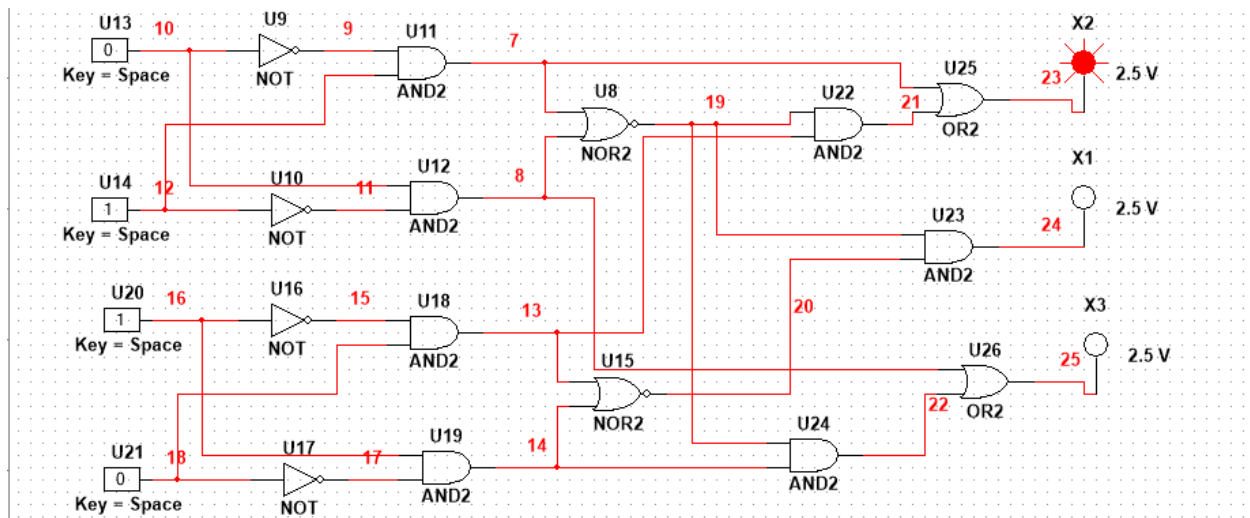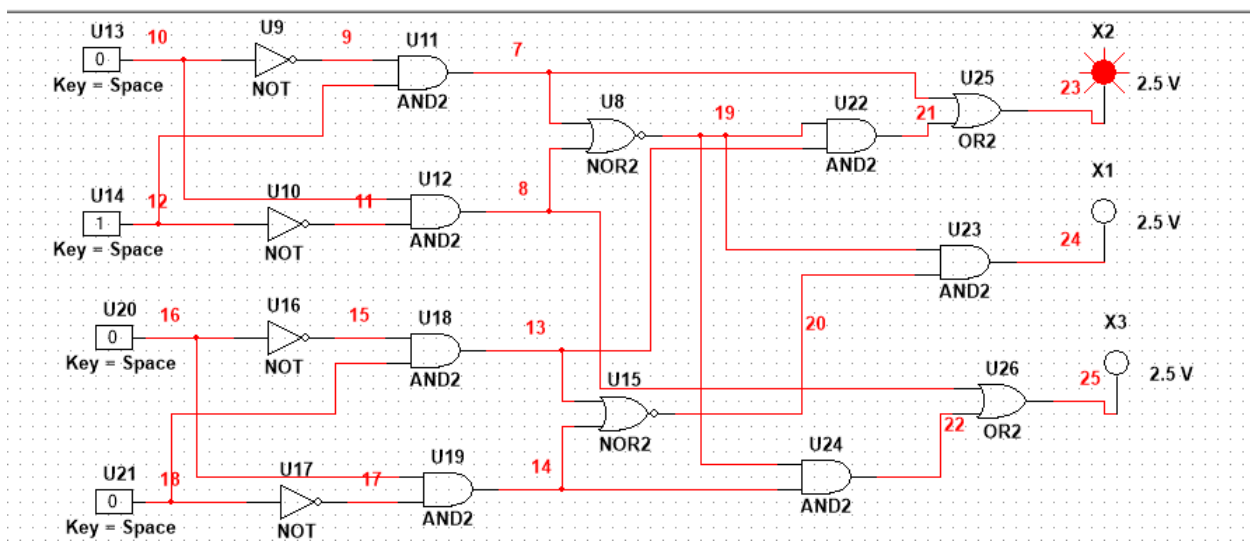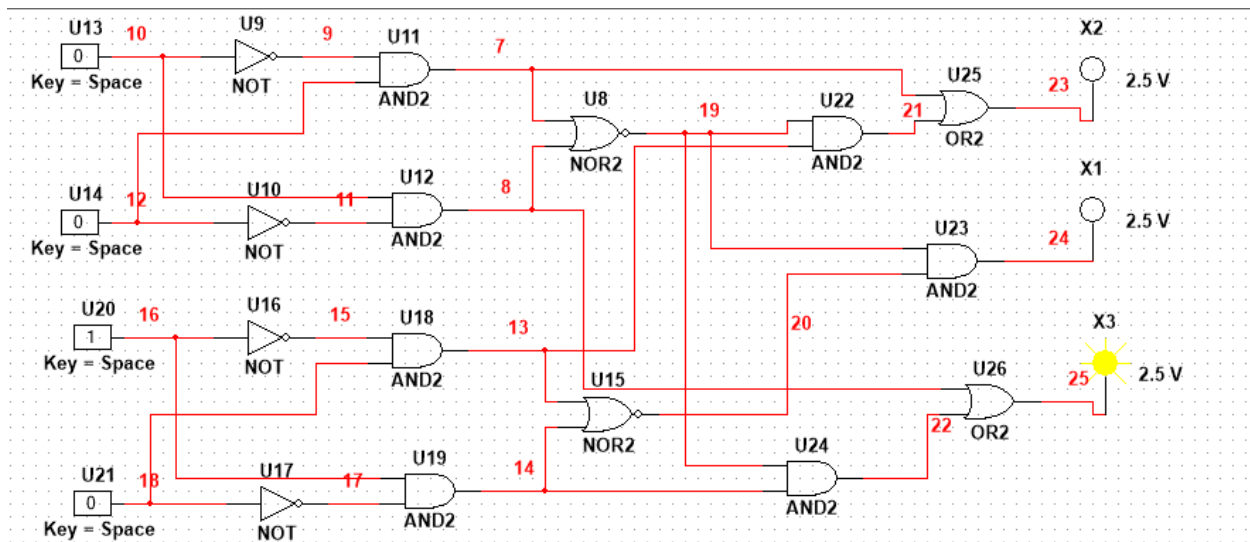

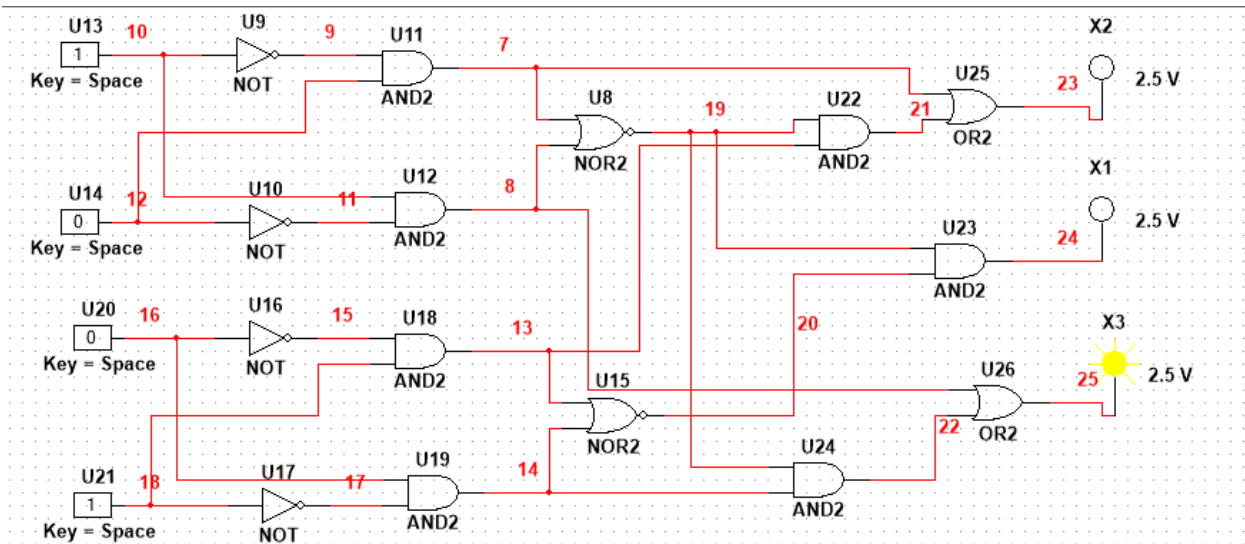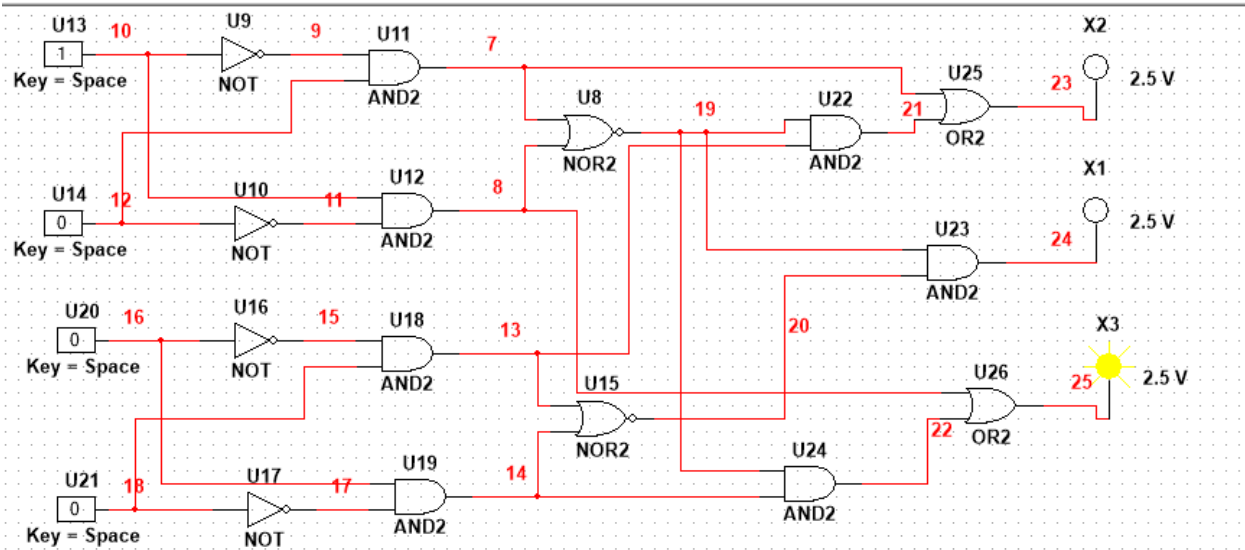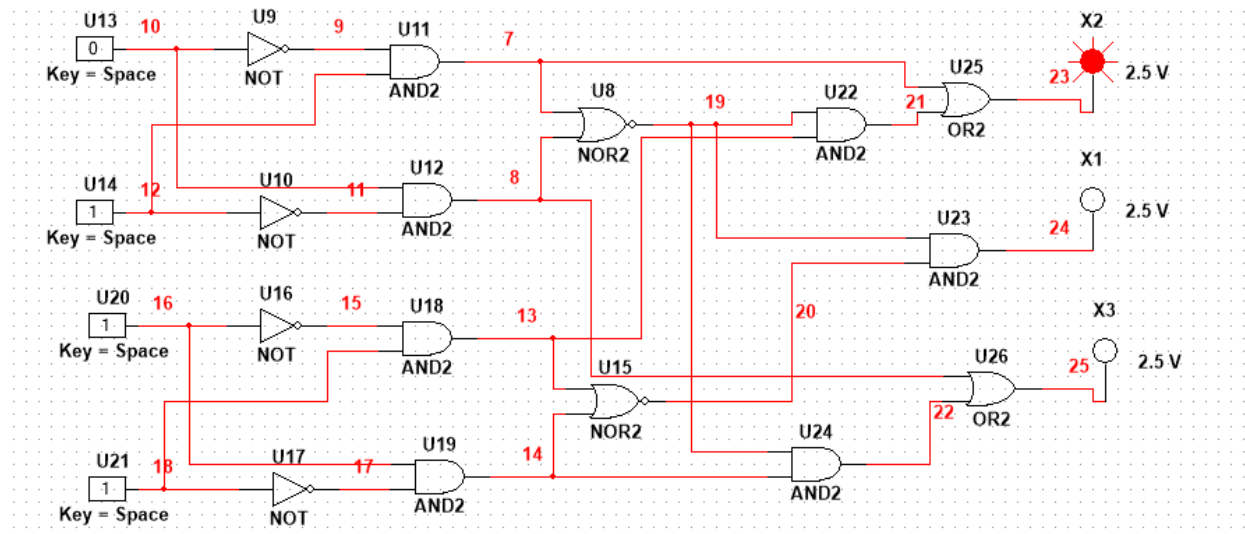



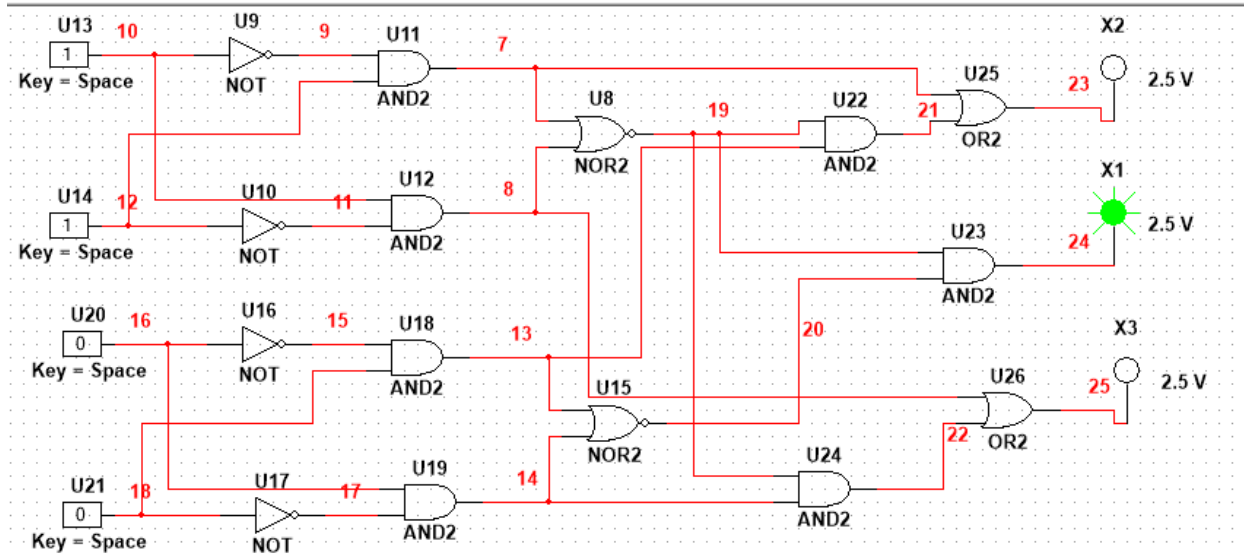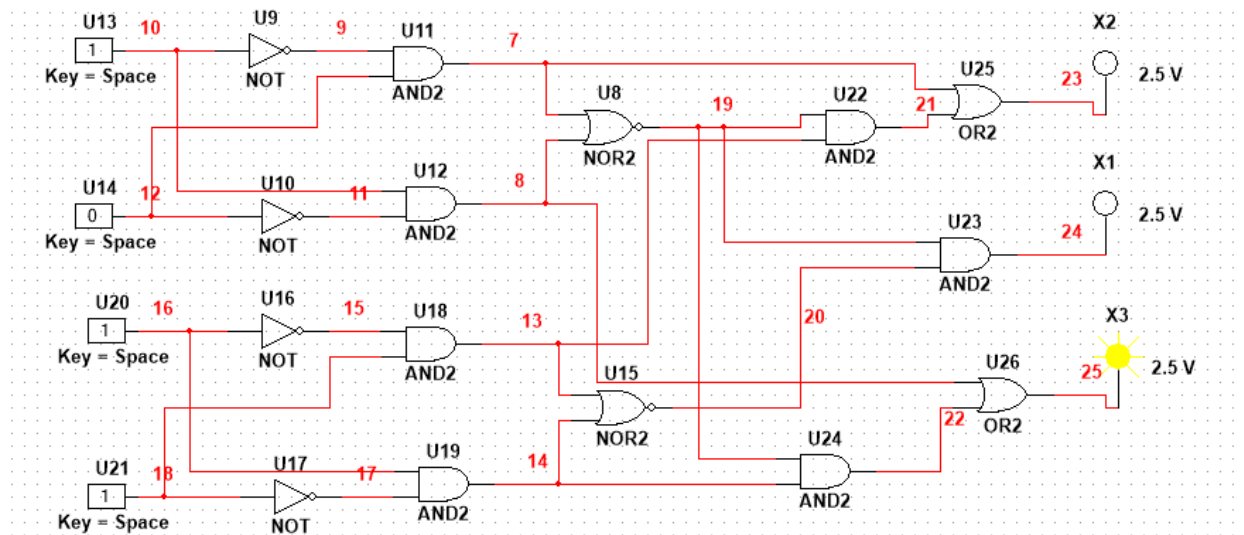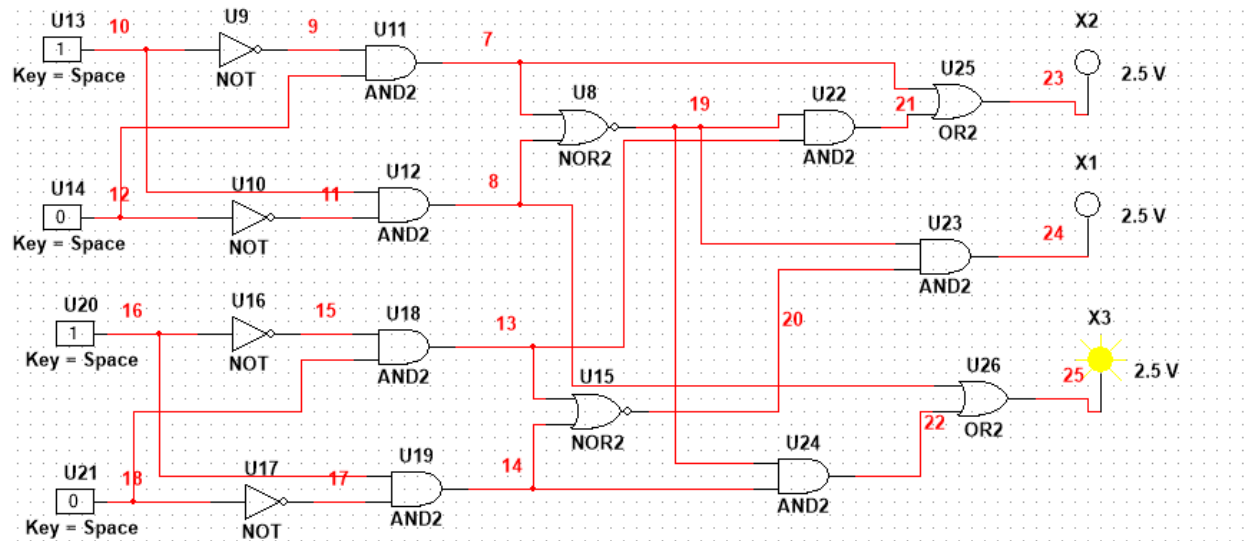

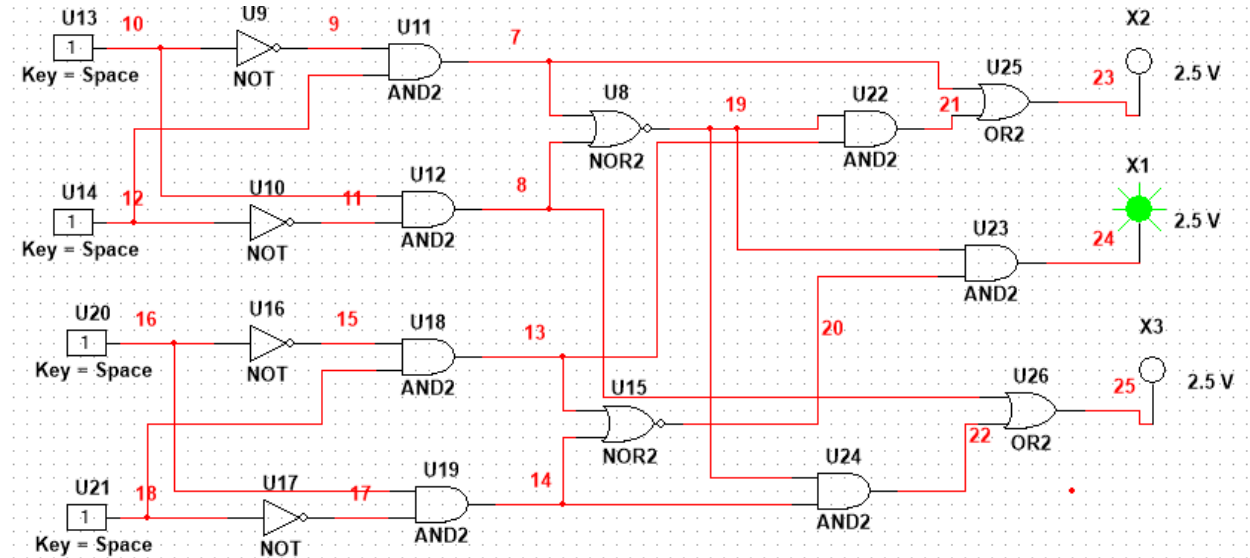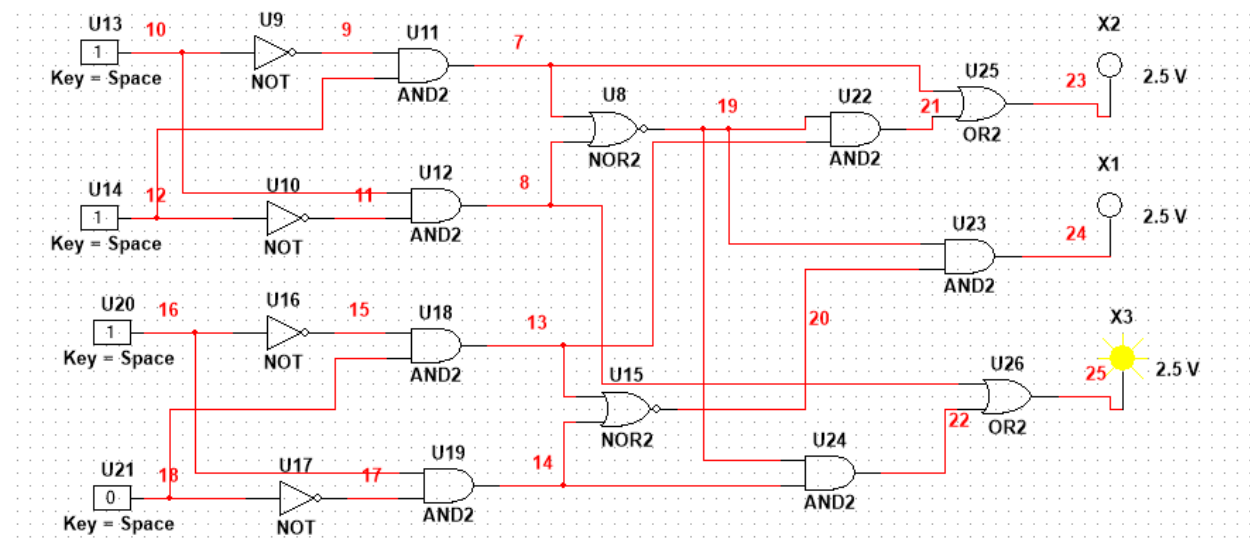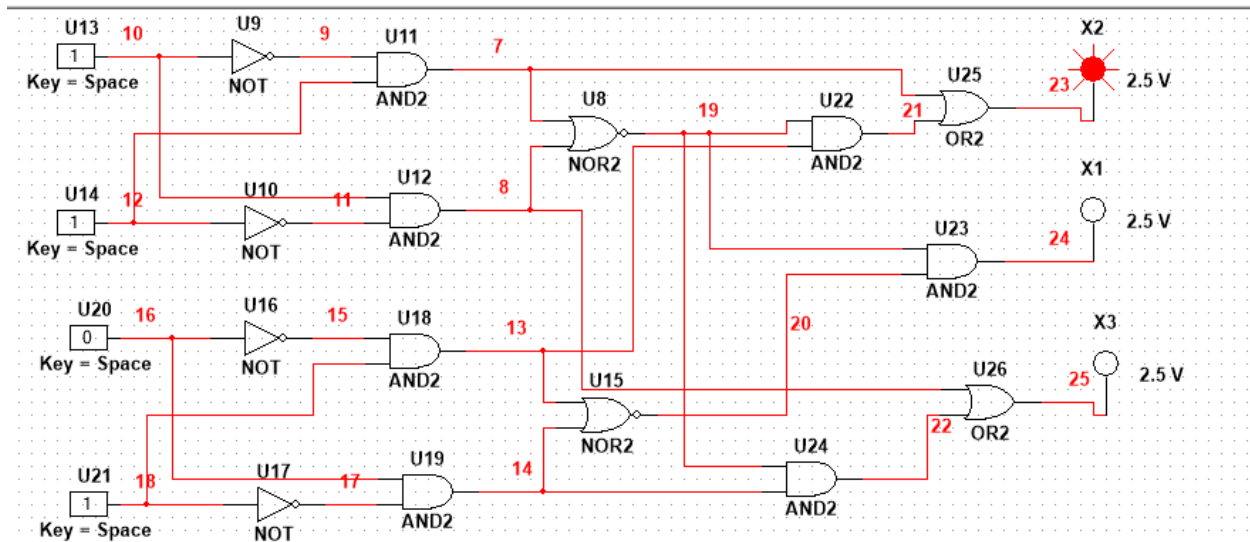

### Discussion:

The experiment is about adder, subtractor and comparator. Adder is used for summing up various kind of digital logic and subtractor is used for various kind of subtraction. Comparator mainly compares the largest voltage among others. In this experiment, we mainly first build a truth table and follows the circuit output from trainer board from various kinds of input. We mainly built half adder, full adder, half subtractor, full subtractor and comparators.

While building the circuit we find out that some IC pins were defected. Also, inside the ~~the~~ breadboard, some alignment was not perfect.

But at the end, we find out the output which was matched with the truth tables. So, we can say that our goal of the experiment were successful.

### Conclusion:

To verify the adder, subtractor and comparator, we have mainly used IC 7408, IC 7432 and IC 7401. We solved a boolean function for developing the truth table. The output was verified.

### Remarks:

- (i) Adders are mainly used for adding some boolean logic and subtractor are used for subtraction of boolean logic.
- (ii) Comparators are used for comparing voltages.
- (iii) Adder and subtractor are mainly used for arithmetic operation and comparator is used for computer logic.

### Reference:

- [1] Thomas: L. Floyd "Digital Fundamentals," 11th edition, 2015.

